



# **L2: Combinational Logic Design: Construction and Boolean Algebra**




**Corrected version – Sept. 7, 2003**



Some (most) lecture material derived from R. Katz, *“Contemporary Logic Design”*, Addison Wesley Publishing Company, Reading, MA, 1993. *Some slides are derived from slides used in past terms of 6.111*



# The Inverter

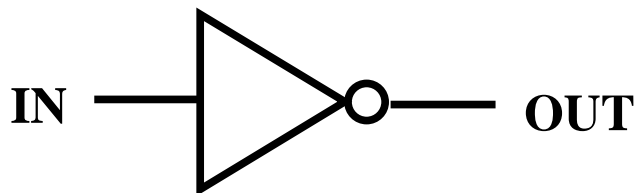

IN	OUT
0	1
1	0

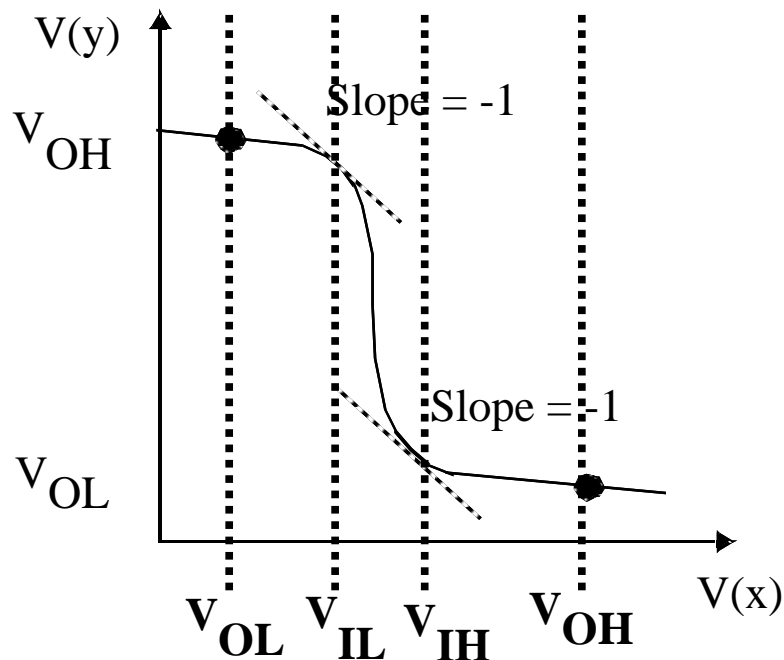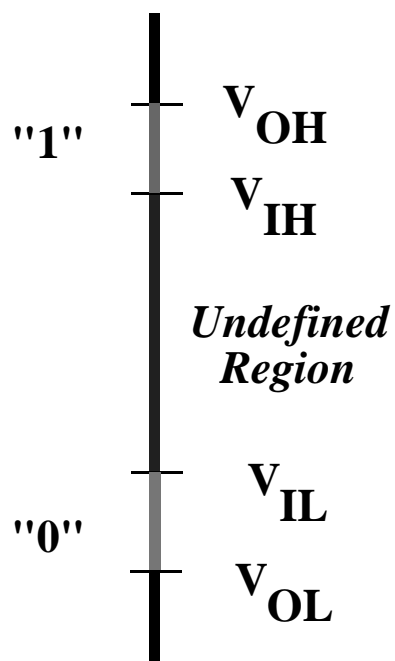






$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

- Large noise margins protect against various noise sources.




# TTL Logic Style (1970's early 80's)

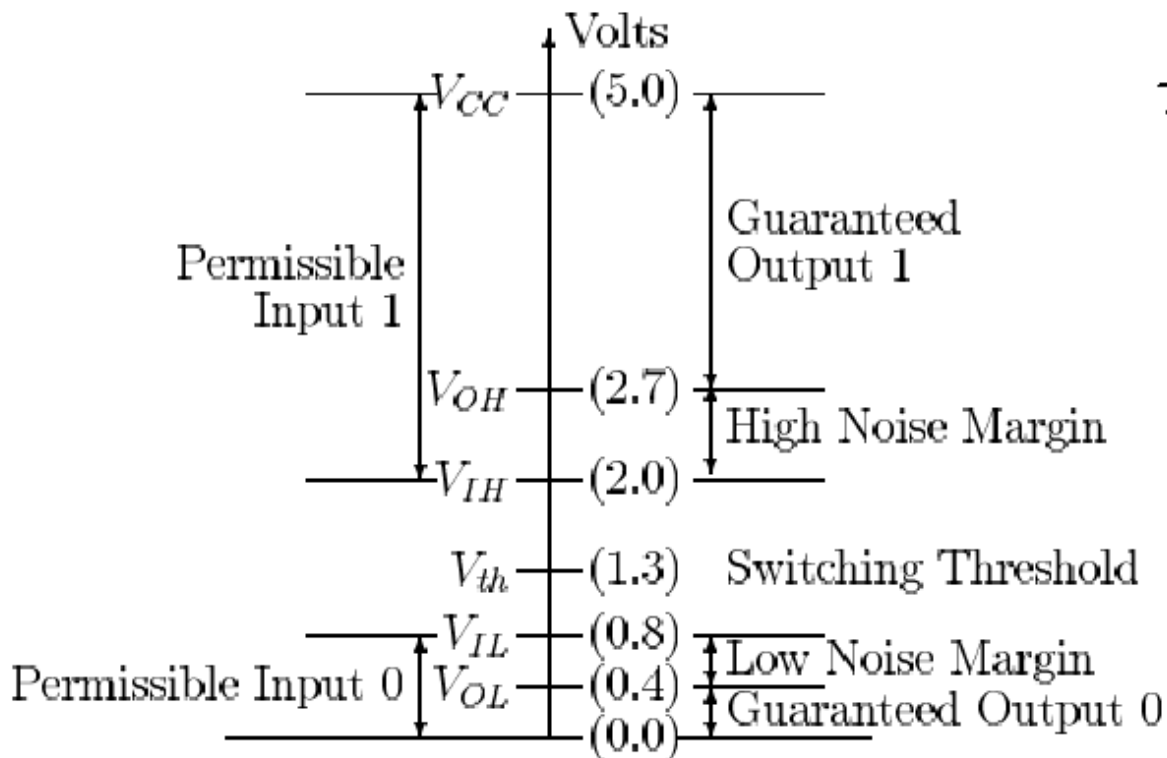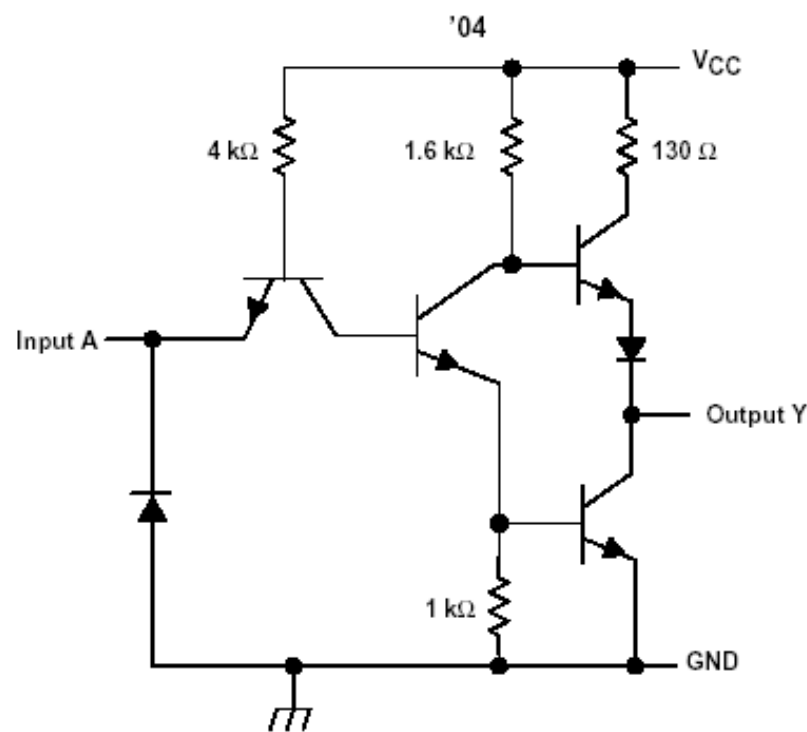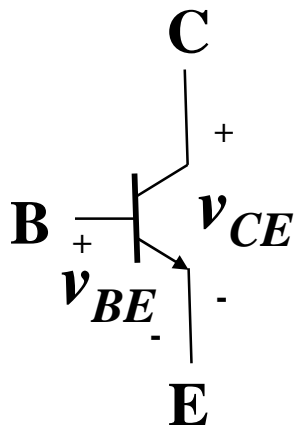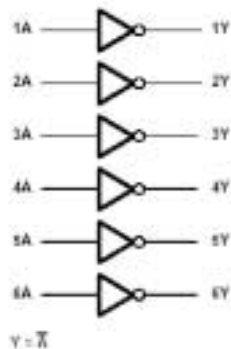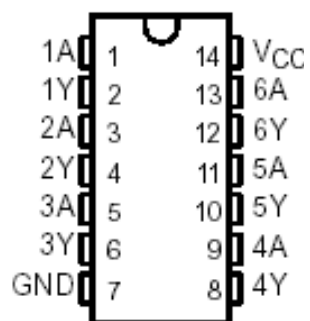

**74LS04**  
(courtesy TI)



# Busses

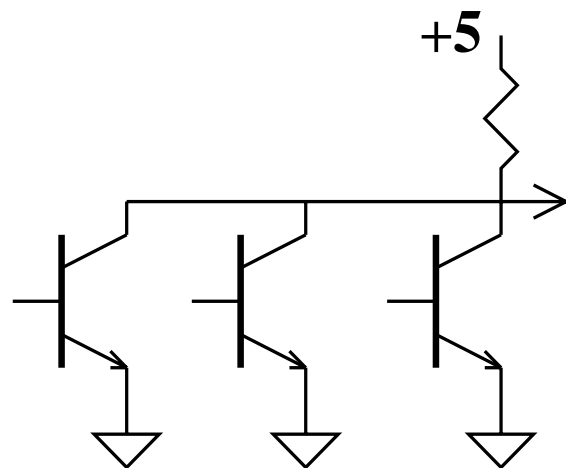


**Open collector gates can be wired together like this to make wired ANDs.**

**This is a bus because it can be driven by more than one source.**



**You can't do this with Totem Pole outputs!**

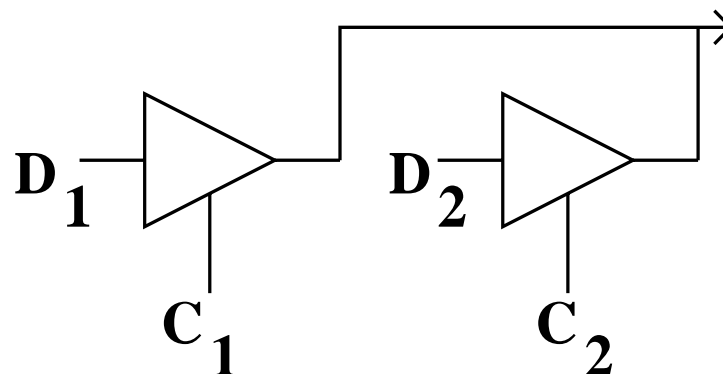**By controlling the gates on both transistors of a Totem Pole to be open, a high impedance is created (this is a tri-state). Control inputs  $C_1$  and  $C_2$  are output enables.**






# MOS Technology: The NMOS Switch

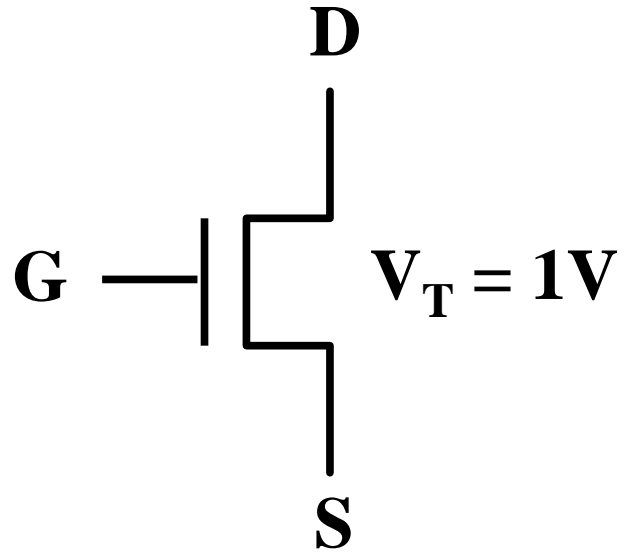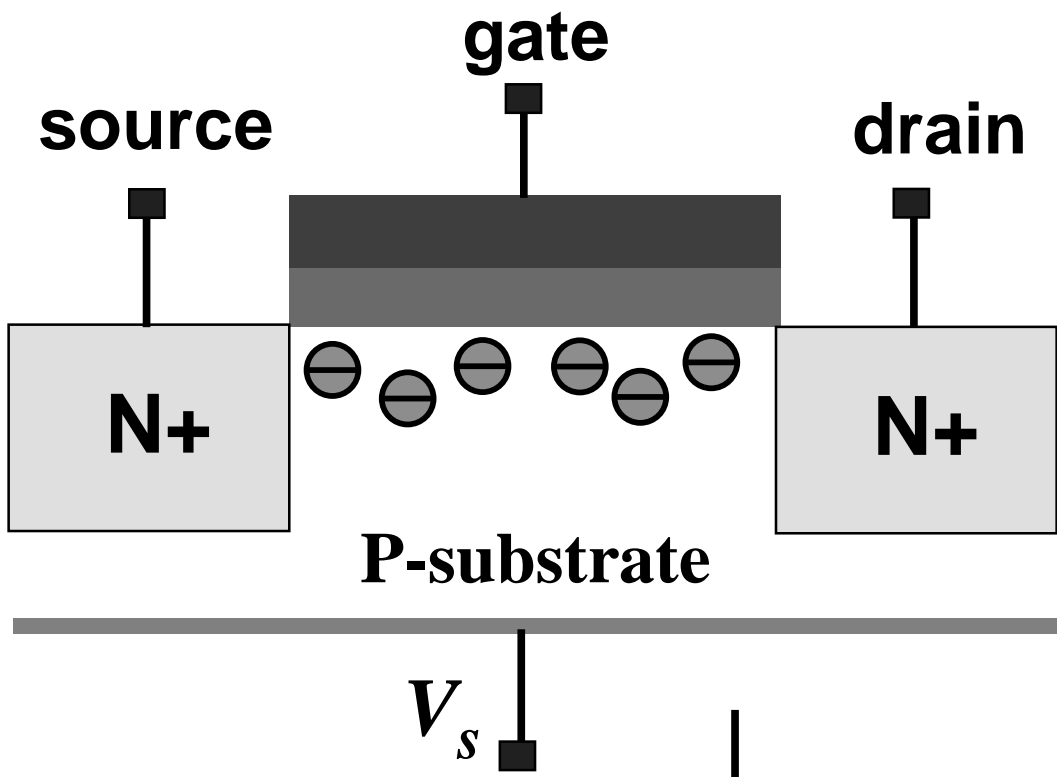


**Switch Model**

OFF

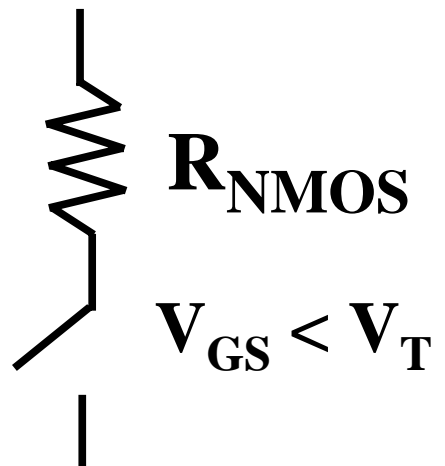



ON

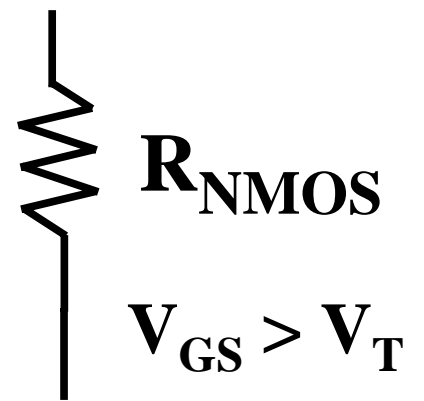

***NMOS ON when Switch Input is High***




# PMOS: The Complementary Switch

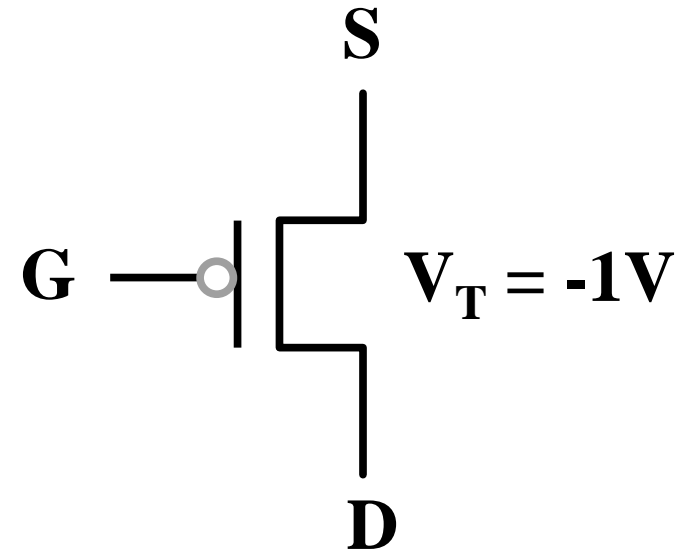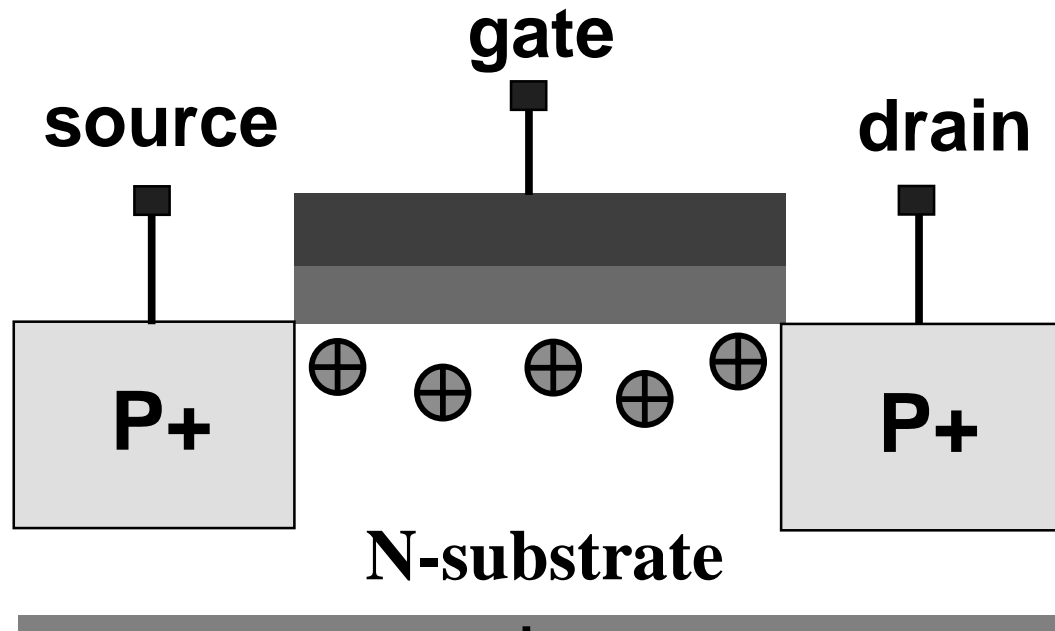


**Switch Model**

OFF

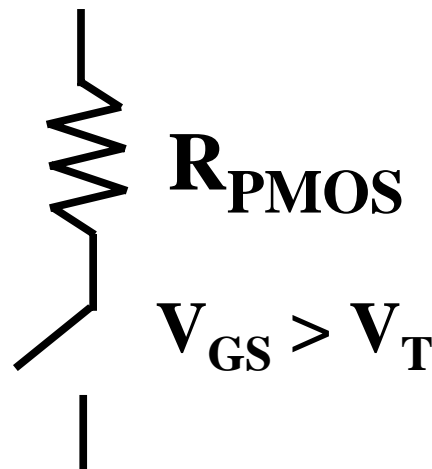


ON

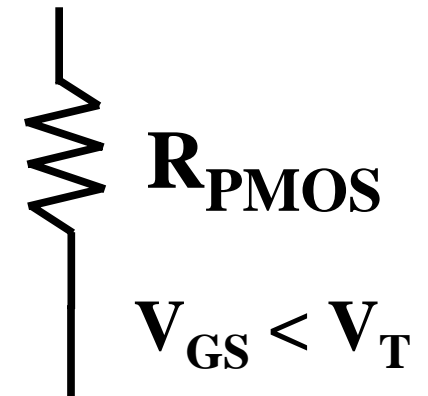


***PMOS ON when Switch Input is Low***



# The CMOS Inverter

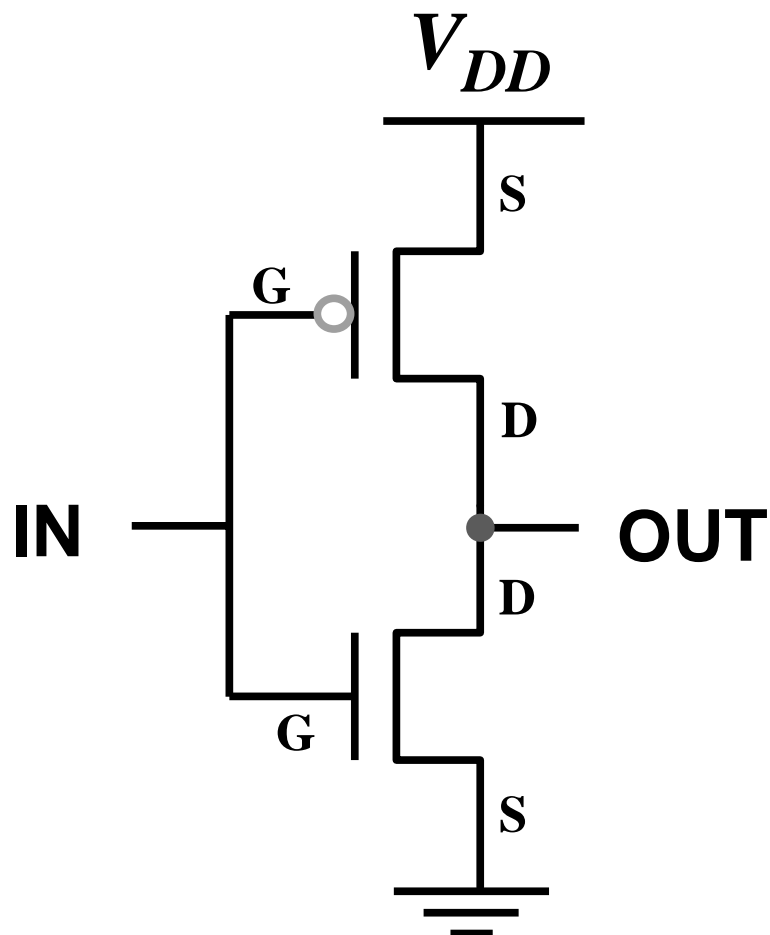

## Switch Model

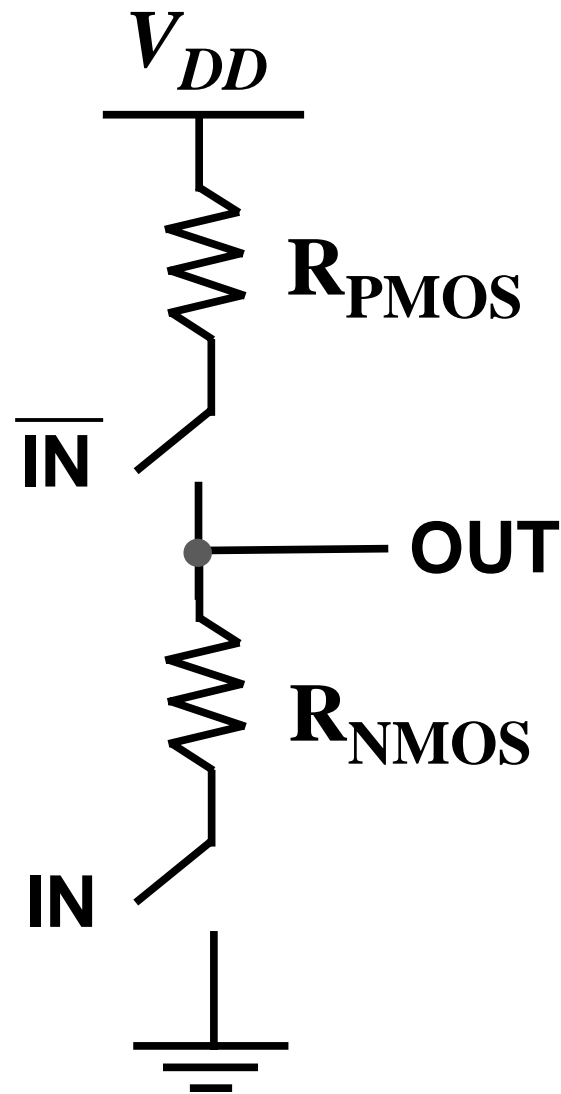



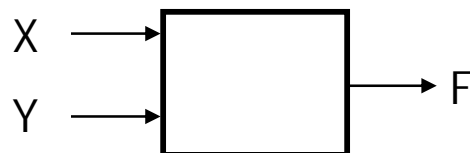
# Possible Function of Two Inputs



There are 16 possible functions of 2 input variables:



X	Y	16 possible functions ( $F_0$ - $F_{15}$ )															
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
		X AND Y		X	Y	X XOR Y		X OR Y		X NOR Y NOT (X OR Y)		X = Y		NOT Y	NOT X	X NAND Y NOT (X AND Y)	

In general, there are  $2^{(2^n)}$  functions of n inputs.



# Common Logic Gates




**Gate**

**Symbol**

**Truth Table**

**Expression**


**NAND**

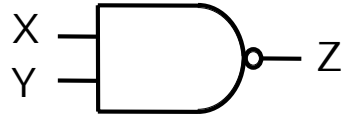

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

$$Z = \overline{X \cdot Y}$$


**AND**

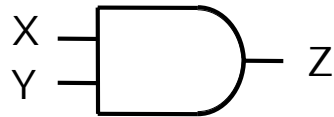

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

$$Z = X \cdot Y$$


**NOR**

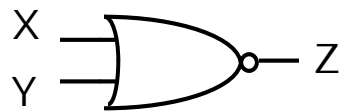

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

$$Z = \overline{X + Y}$$

**OR**

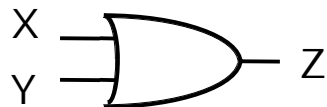

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1


$$Z = X + Y$$



# Exclusive (N)OR Gate




**XOR**  
 $(X \oplus Y)$

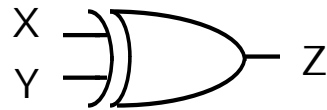

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

$Z = X \bar{Y} + \bar{X} Y$   
 X or Y but not both  
 ("inequality", "difference")

**XNOR**  
 $\overline{(X \oplus Y)}$

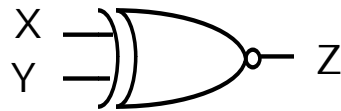


X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

$Z = \bar{X} \bar{Y} + X Y$   
 X and Y the same  
 ("equality")

*Widely used in arithmetic structures such as adders and multipliers*




# Generic CMOS Recipe

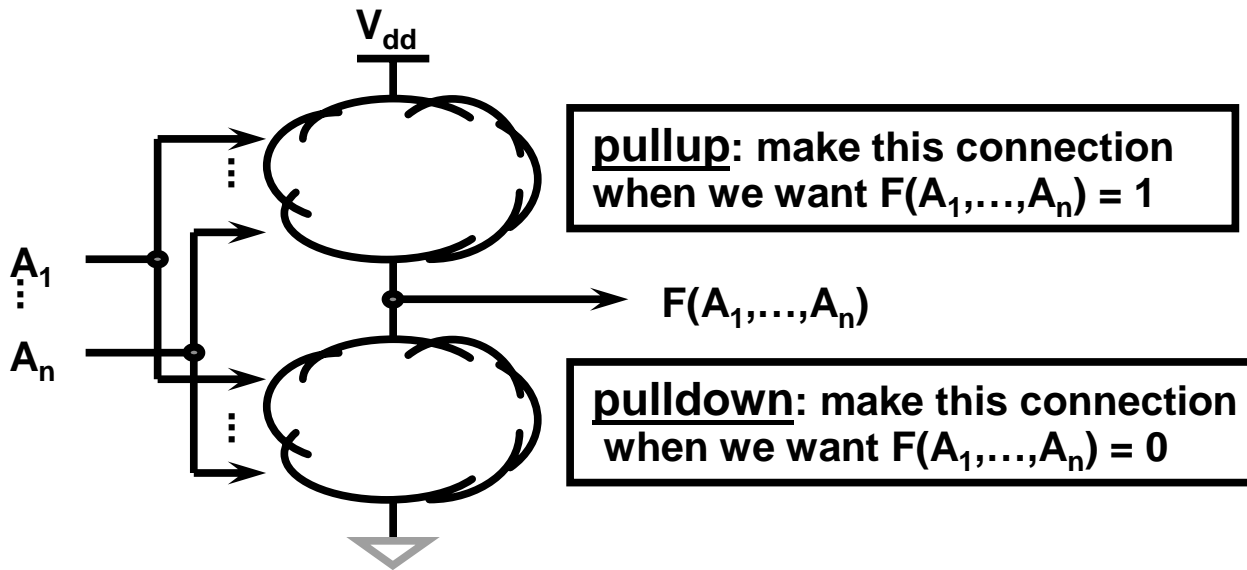

**Note: CMOS gates result in inverting functions!**

**(easier to build NAND vs. AND)**

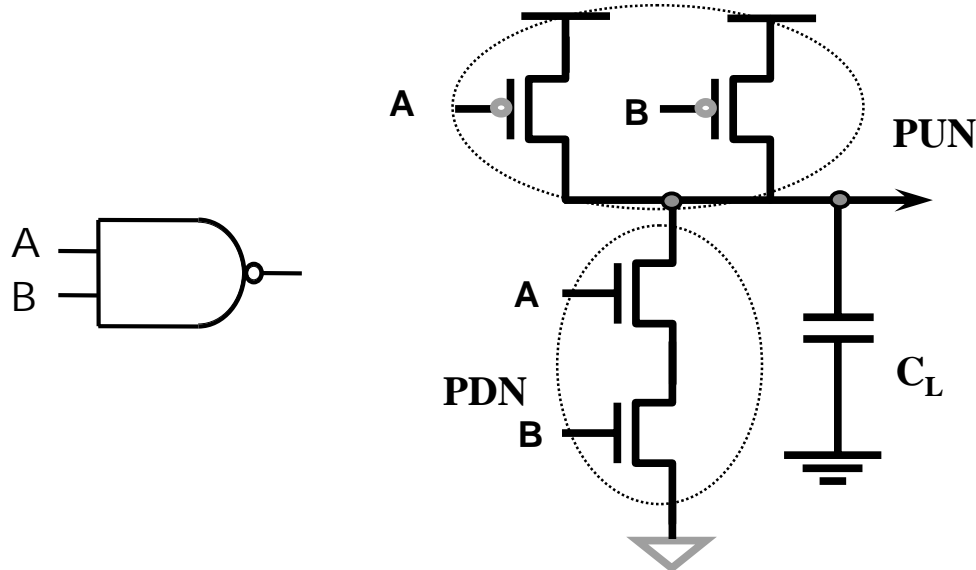

A	B	PDN	PUN	O
0	0	Off	On	1
0	1	Off	On	1
1	0	Off	On	1
1	1	On	Off	0

**How do you build a 2 input NOR Gate?**



# Theorems of Boolean Algebra (I)



## ■ Elementary

1.  $X + 0 = X$

2.  $X + 1 = 1$

3.  $X + X = X$

4.  $\overline{\overline{X}} = X$

5.  $X + \overline{X} = 1$

1D.  $X \cdot 1 = X$

2D.  $X \cdot 0 = 0$

3D.  $X \cdot X = X$

5D.  $X \cdot \overline{X} = 0$

## ■ Commutativity:

6.  $X + Y = Y + X$

6D.  $X \cdot Y = Y \cdot X$

## ■ Associativity:

7.  $(X + Y) + Z = X + (Y + Z)$

7D.  $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$

## ■ Distributivity:

8.  $X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$

8D.  $X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$

## ■ Uniting:

9.  $X \cdot Y + X \cdot \overline{Y} = X$

9D.  $(X + Y) \cdot (X + \overline{Y}) = X$

## ■ Absorption:

10.  $X + X \cdot Y = X$

10D.  $X \cdot (X + Y) = X$

11.  $(X + \overline{Y}) \cdot Y = X \cdot Y$

11D.  $(X \cdot \overline{Y}) + Y = X + Y$



# Theorems of Boolean Algebra (II)



## ■ Factoring:

$$12. (X \cdot Y) + (X \cdot Z) = X \cdot (Y + Z)$$

$$12D. (X + Y) \cdot (X + Z) = X + (Y \cdot Z)$$

## ■ Consensus:

$$13. (X \cdot Y) + (Y \cdot Z) + (\bar{X} \cdot Z) = X \cdot Y + \bar{X} \cdot Z$$

$$13D. (X + Y) \cdot (Y + Z) \cdot (\bar{X} + Z) = (X + Y) \cdot (\bar{X} + Z)$$

## ■ De Morgan's:

$$14. \overline{(X + Y + \dots)} = \bar{X} \cdot \bar{Y} \cdot \dots$$

$$14D. \overline{(X \cdot Y \cdot \dots)} = \bar{X} + \bar{Y} + \dots$$

## ■ Generalized De Morgan's:

$$15. \overline{f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)} = f(\bar{X}_1, \bar{X}_2, \dots, \bar{X}_n, 1, 0, \cdot, +)$$

## ■ Duality

- Dual of a Boolean expression is derived by replacing  $\cdot$  by  $+$ ,  $+$  by  $\cdot$ ,  $0$  by  $1$ , and  $1$  by  $0$ , and leaving variables unchanged
- $f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) \Leftrightarrow f(\bar{X}_1, \bar{X}_2, \dots, \bar{X}_n, 1, 0, \cdot, +)$




# Simple Example: One Bit Adder


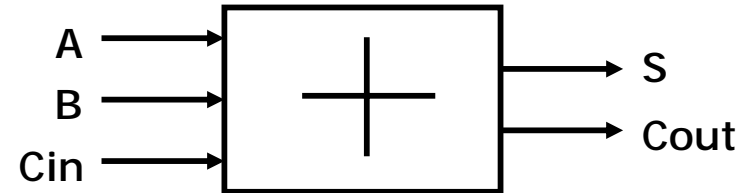
## ■ 1 bit binary adder

- inputs: A, B, Carry in
- outputs: Sum, Carry out



A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## Sum-of-Products Canonical Form

$$S = \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in}$$

$$C_{out} = \bar{A} B C_{in} + A \bar{B} C_{in} + A B \bar{C}_{in} + A B C_{in}$$

## ■ Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- Each variable appears exactly once, in true or inverted form (but not both).



# Simplify Boolean Expressions



$$\begin{aligned} \text{Cout} &= \overline{A} B C_{in} + A \overline{B} C_{in} + A B \overline{C}_{in} + A B C_{in} \\ &= \overline{A} B C_{in} + A B C_{in} + A \overline{B} C_{in} + A B C_{in} + A B \overline{C}_{in} + A B C_{in} \\ &= (\overline{A} + A) B C_{in} + A (\overline{B} + B) C_{in} + A B (\overline{C}_{in} + C_{in}) \\ &= B C_{in} + A C_{in} + A B \\ &= (B + A) C_{in} + A B \end{aligned}$$

$$\begin{aligned} S &= \overline{A} \overline{B} C_{in} + \overline{A} B \overline{C}_{in} + A \overline{B} \overline{C}_{in} + A B C_{in} \\ &= (\overline{A} \overline{B} + A B) C_{in} + (A \overline{B} + \overline{A} B) \overline{C}_{in} \\ &= \overline{(A \oplus B)} C_{in} + (A \oplus B) \overline{C}_{in} \\ &= A \oplus B \oplus C_{in} \end{aligned}$$



# Sum of Products & Product of Sums



- Product term (or minterm): ANDed product of literals – input combination for which output is true

A	B	C	minterms	
0	0	0	$\overline{A} \overline{B} \overline{C}$	m0
0	0	1	$\overline{A} \overline{B} C$	m1
0	1	0	$\overline{A} B \overline{C}$	m2
0	1	1	$\overline{A} B C$	m3
1	0	0	$A \overline{B} \overline{C}$	m4
1	0	1	$A \overline{B} C$	m5
1	1	0	$A B \overline{C}$	m6
1	1	1	$A B C$	m7

F in canonical form:

$$F(A, B, C) = \Sigma m(1,3,5,6,7)$$

$$= m1 + m3 + m5 + m6 + m7$$

$$F = \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} C + A B \overline{C} + ABC$$

canonical form  $\neq$  minimal form

$$F(A, B, C) = \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} C + ABC + ABC \overline{C}$$

$$= (\overline{A} \overline{B} + \overline{A} B + A \overline{B} + AB)C + ABC \overline{C}$$

$$= ((\overline{A} + A)(\overline{B} + B))C + ABC \overline{C}$$

$$= C + ABC \overline{C} = ABC \overline{C} + C = AB + C$$

short hand notation form in terms of 3 variables

- Sum term (or maxterm): ORed sum of literals – input combination for which output is false

A	B	C	maxterms	
0	0	0	$A + B + C$	M0
0	0	1	$A + B + \overline{C}$	M1
0	1	0	$A + \overline{B} + C$	M2
0	1	1	$A + \overline{B} + \overline{C}$	M3
1	0	0	$\overline{A} + B + C$	M4
1	0	1	$\overline{A} + B + \overline{C}$	M5
1	1	0	$\overline{A} + \overline{B} + C$	M6
1	1	1	$\overline{A} + \overline{B} + \overline{C}$	M7

F in canonical form:

$$F(A, B, C) = \Pi M(0,2,4)$$

$$= M0 \cdot M2 \cdot M4$$

$$= (A + B + C) (A + \overline{B} + C) (\overline{A} + B + C)$$

canonical form  $\neq$  minimal form

$$F(A, B, C) = (A + B + C) (A + \overline{B} + C) (\overline{A} + B + C)$$

$$= (A + B + C) (A + \overline{B} + C)$$

$$(A + B + C) (\overline{A} + B + C)$$

$$= (A + C) (B + C)$$

short hand notation for maxterms of 3 variables



# Mapping Between Forms



1. **Minterm to Maxterm conversion:**  
rewrite minterm shorthand using maxterm shorthand  
replace minterm indices with the indices not already used

$$\text{E.g., } F(A,B,C) = \Sigma m(3,4,5,6,7) = \Pi M(0,1,2)$$

2. **Maxterm to Minterm conversion:**  
rewrite maxterm shorthand using minterm shorthand  
replace maxterm indices with the indices not already used

$$\text{E.g., } F(A,B,C) = \Pi M(0,1,2) = \Sigma m(3,4,5,6,7)$$

3. **Minterm expansion of F to Minterm expansion of F':**  
in minterm shorthand form, list the indices not already used in F

$$\begin{array}{lcl} \text{E.g., } F(A,B,C) = \Sigma m(3,4,5,6,7) & \longrightarrow & F'(A,B,C) = \Sigma m(0,1,2) \\ & \longrightarrow & = \Pi M(3,4,5,6,7) \\ & & = \Pi M(0,1,2) \end{array}$$

4. **Minterm expansion of F to Maxterm expansion of F':**  
rewrite in Maxterm form, using the same indices as F

$$\begin{array}{lcl} \text{E.g., } F(A,B,C) = \Sigma m(3,4,5,6,7) & \longrightarrow & F'(A,B,C) = \Pi M(3,4,5,6,7) \\ & \longrightarrow & = \Sigma m(0,1,2) \\ & & = \Pi M(0,1,2) \end{array}$$



# The Uniting Theorem



- Key tool to simplification:  $A(\bar{B} + B) = A$
- Essence of simplification of two level logic
  - Find two element subsets of the ON set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements

$$F = \bar{A}\bar{B} + A\bar{B} = (\bar{A} + A)\bar{B} = \bar{B}$$

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

B has the same value in both on set rows  
 - B remains

A has a different value in the two rows  
 - A is eliminated



# Karnaugh Maps



- Alternative to truth tables to help visualize adjacencies
  - Guide to applying the uniting theorem- On set elements with only one variable changing value are adjacent unlike in a linear truth table

A	0	1
B	0	1
0	1	2
1	0	3

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

- Numbering scheme based on Gray-code

- e.g., 00, 01, 11, 10 (only a single bit changes in code for adjacent map cells)

**2 variable K map**

A	0	1
B	0	1
0	0	2
1	1	3

**3 variable K map**

AB	00	01	11	10
C	0	1	3	2
0	0	2	6	4
1	1	3	7	5

AB	00	01	11 00	
CD	00	01	11	00
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

**4 variable K map**



# K Map Examples



		A			
		00	01	11	10
C	AB	00	01	11	10
	0	0	0	1	1
1	0	0	1	1	

**F(A,,C) =**

		A			
		00	01	11	10
C	AB	00	01	11	10
	0	1	0	0	1
1	0	0	1	1	

**F(A,B,C) =  $\Sigma m(0,4,5,7)$**

**F =**

		A			
		00	01	11	10
Cin	A B	00	01	11	10
	0	0	0	1	0
1	0	1	1	1	

**Cout =**

		A			
		00	01	11	10
C	AB	00	01	11	10
	0	0	1	1	0
1	1	1	0	0	


**F' simply replace 1s with 0s and vice versa**

**F'(A,B,C) =  $\Sigma m(1,2,3,6)$**

**F' =**



# Four Variable Karnaugh Map

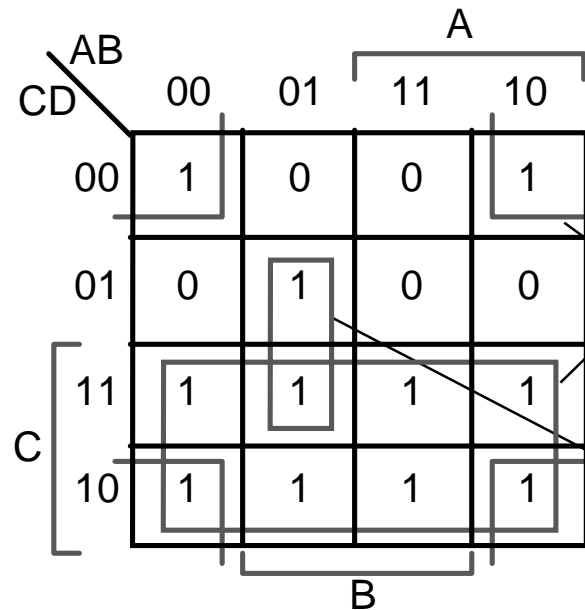

$$F(A,B,C,D) = \sum m(0,2,3,5,6,7,8,10,11,14,15)$$

$$F = C + \bar{A} B D + \bar{B} \bar{D}$$

Find the smallest number of the largest possible groupings that cover the ON set.



# K Map Example: Don't Cares



**Don't Cares can be treated as 1s or 0s if it is advantageous to do so.**

		AB		A	
		00	01	11	10
C	CD	00	01	11	10
	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0
		B		D	

$$F(A,B,C,D) = \sum m(1,3,5,7,9) + \sum d(6,12,13)$$

$$F = \bar{A} D + \bar{B} \bar{C} D \text{ w/o don't cares}$$

$$F = \bar{C} D + \bar{A} D \text{ w/ don't cares}$$

By treating this don't care as a "1", a group of 4 can be used instead of a group of 2.

In PoS form:  $F = D (\bar{A} + \bar{C})$

Equivalent answer as above,  
but fewer literals

		AB		A	
		00	01	11	10
C	CD	00	01	11	10
	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0
		B		D	




# Hazards




**Static Hazards: Consider this function:**

$$F = A * \bar{C} + B * C$$

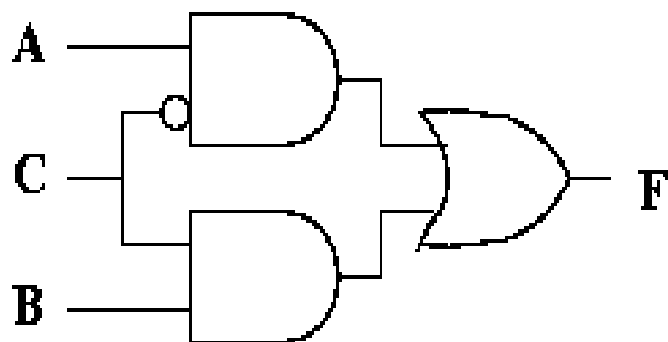


	AB			
C	00	01	11	10
0	0	0	1	1
1	0	1	1	0

**A = B = 1**

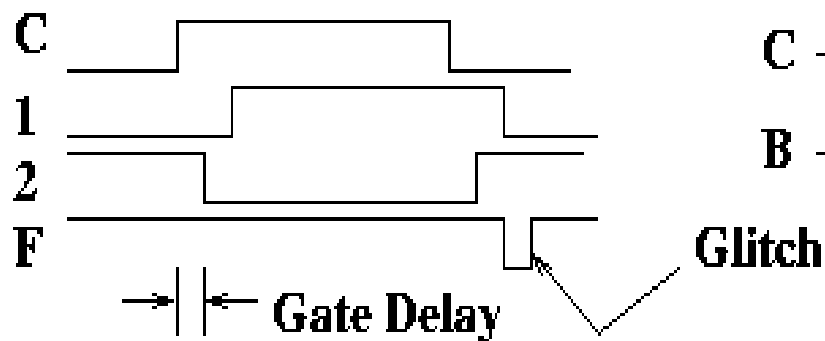

**Implemented with MSI gates:**

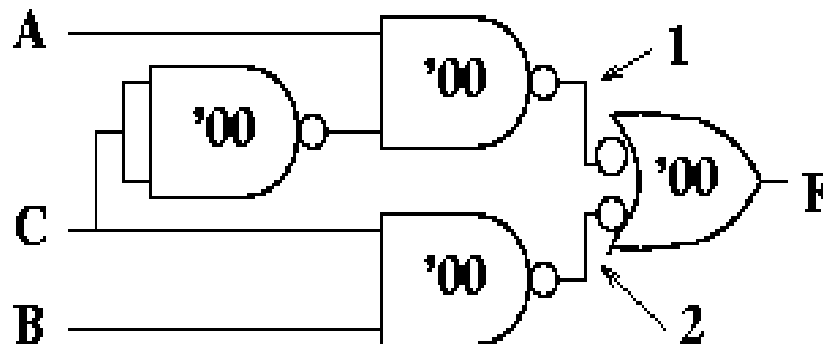



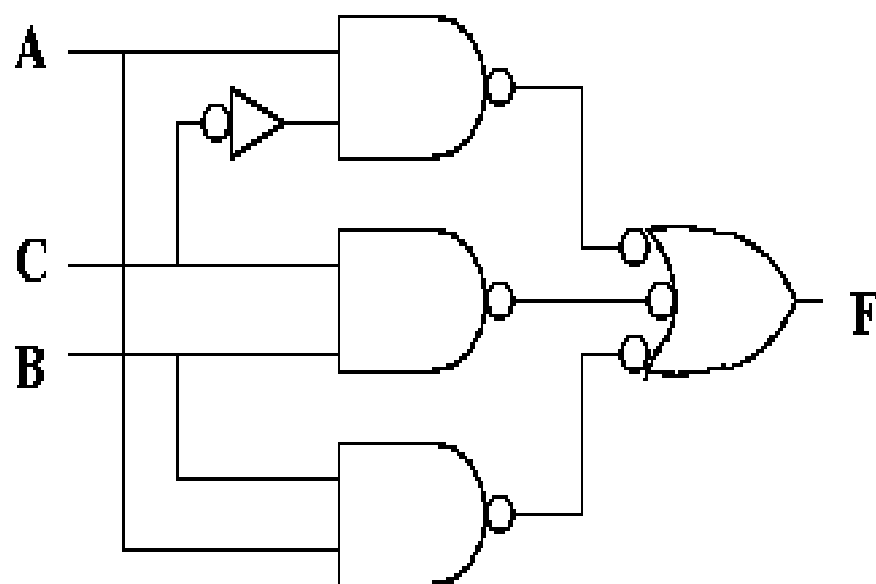
# Fixing Hazards



The glitch is the result of timing differences in parallel data paths. It is associated with the function jumping between groupings or product terms on the K-map. To fix it, cover it up with another grouping or product term!



		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	0

$$F = A * \bar{C} + B * C + A * B$$