



Data Transmission



Data Transmission





- **There are two basic methods.**
 - **Recover a clock from a serial transmission.**
 - This requires a phase lock loop.
 - **Examples:**
 - network data
 - disk
 - tape
 - GPS
 - Digital TV
 - We will not do this in 6.111.
 - FPGAs are hardwired to use a single clock.
 - **Synchronize incoming data to a local clock.**
 - **Serial data transmission**
 - Uses only two wires (or radio and earth ground).
 - Slow – at most one bit per clock period
 - **Parallel data transmission**
 - Uses at least one wire per bit.
 - Fast – a word (n bits) at a time
 - Need to agree on control signals to know when data is stable




Serial Data Transmission



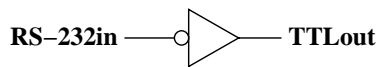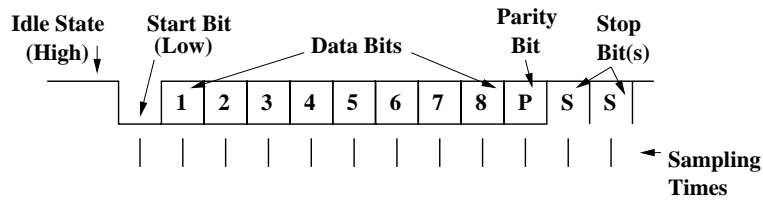- RS – 232 is a serial interface standard.
 - RS – 232 levels are between
 - - 3v and - 15 v for a logic 1
 - + 3v and + 15 v for a logic 0
- The TTL signal below has an “idle” state of a logic 1.
 - MAXIM 233 has two RS – 232 to TTL and two TTL to RS – 232 level converters.




L15 6.111

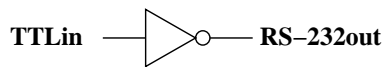

Introductory Digital Systems Laboratory 3





AY-3-1015D Receive Section

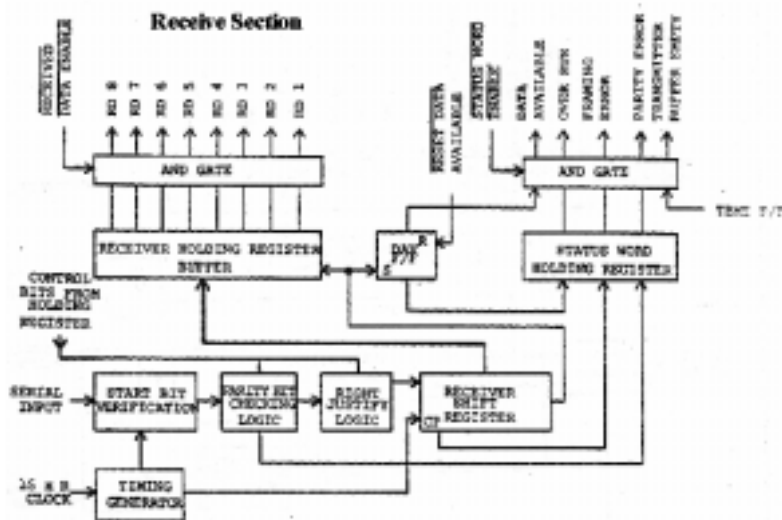


L15 6.111

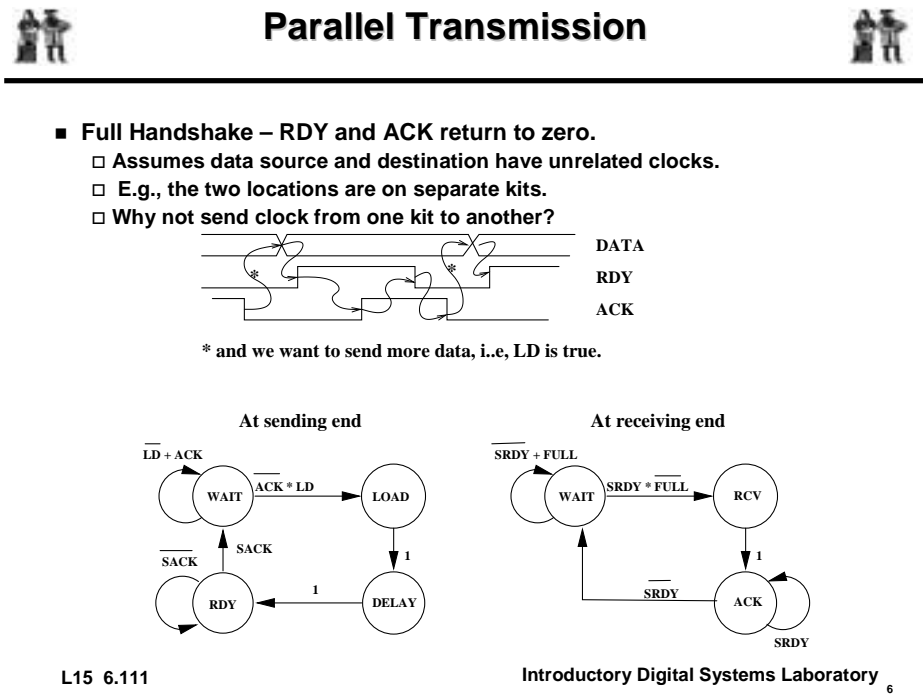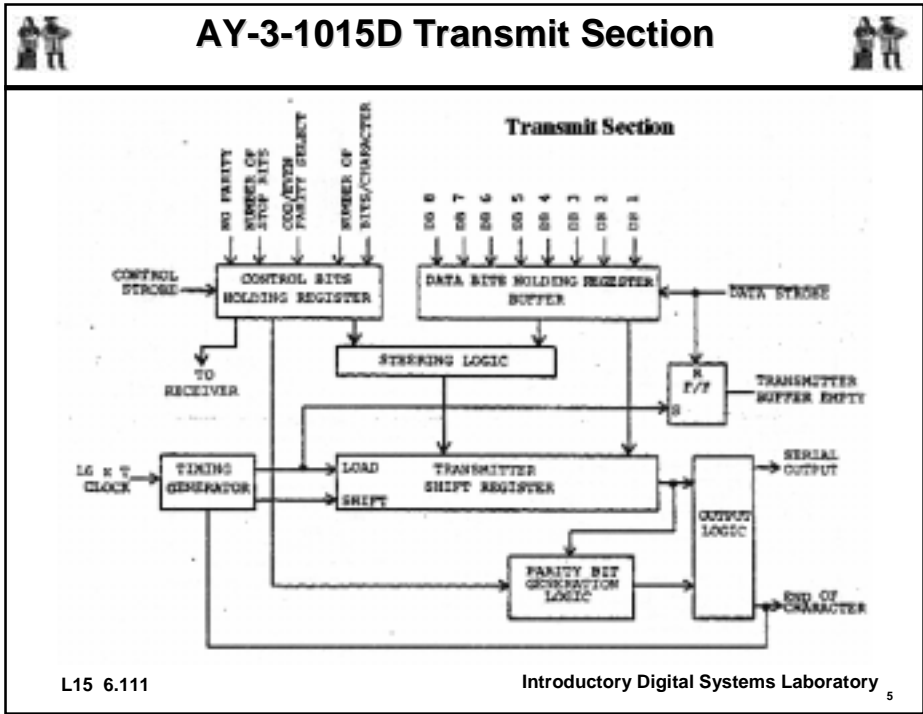Introductory Digital Systems Laboratory 4






Parallel Interface

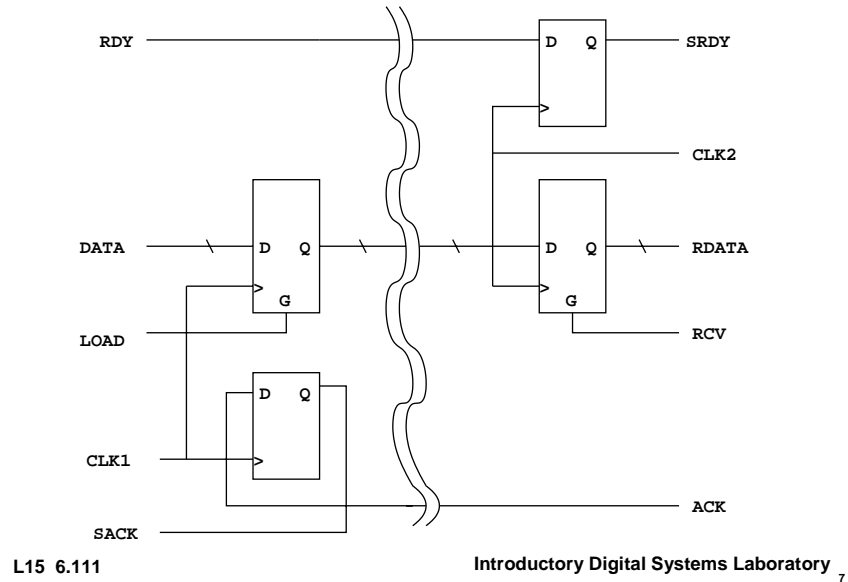

Transmission Lines



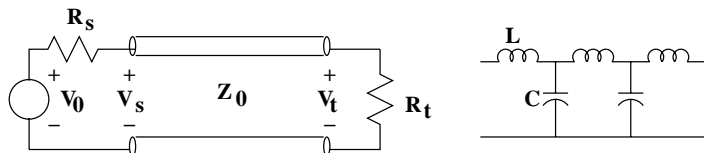- Signals travel on wires.
 - Attenuation – losses due to resistance of wires
 - Reflections – affected by terminations



Transmission line has characteristic parameters:

L: Inductance per unit length
C: Capacitance per unit length

Z_0 : Characteristic Impedance

U_0 : Phase Velocity

$$Z_0 = \sqrt{\frac{L}{C}}$$


$$U_0 = \sqrt{\frac{1}{LC}}$$




Signal Propagation



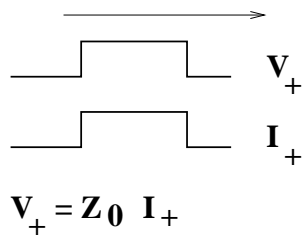- Pulses travel along the line.
 - Ratio of voltage to current is the “characteristic impedance”.
 - Sign of that ratio is the direction of propagation.
 - Pulses propagate at a velocity $< c$ (speed of light).



L15 6.111

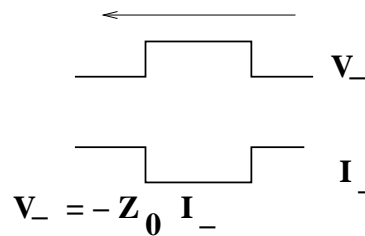


Introductory Digital Systems Laboratory 9




Reflections



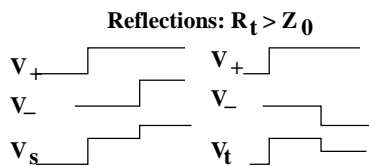- Pulses are absorbed if the receiving end is matched to the characteristic impedance.
 - If the receiving end is not matched then a pulse “reflects”.
 - The sign of the reflection depends on the impedance value relative to the characteristic impedance.



L15 6.111

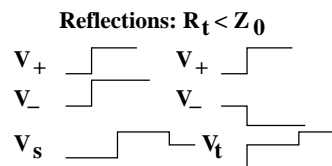


Introductory Digital Systems Laboratory 10



Characteristic Impedance Demo



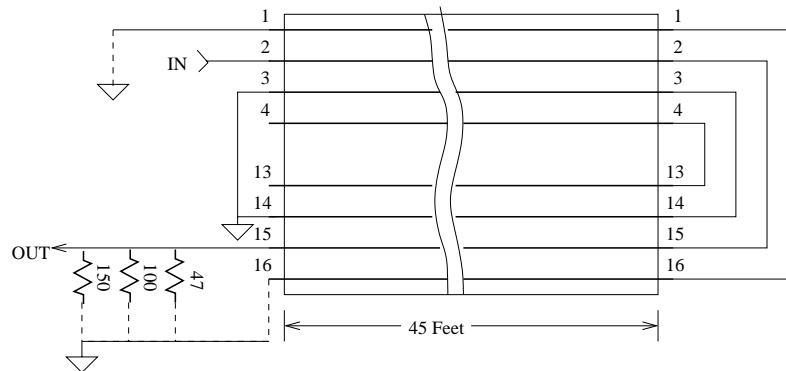- Reflections depend on the terminating impedance.
 - They can be minimized by terminating correctly, i.e., with the characteristic impedance?
 - Why can't they be eliminated?



Moral: Terminate Wires in Characteristic Impedance

L15 6.111


Introductory Digital Systems Laboratory 11



Crosstalk Demo



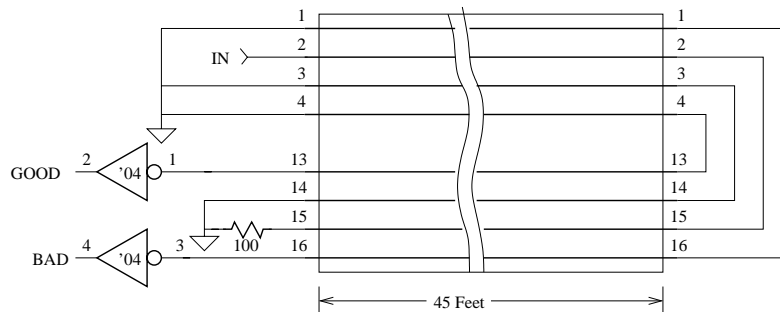- Flat ribbon cable – similar to kit interconnect cables
 - The wires are situated right next to each other.
 - They have capacitive and inductive coupling.
- Crosstalk is minimized by alternating signals and grounds.
 - Ground – Signal – Ground – Signal



Moral: Alternate Ground and Signal Wires in Cables

L15 6.111

Introductory Digital Systems Laboratory 12