



L6: Simple Sequential Examples and VHDL




Acknowledgement: Nathan Ickes



A Simple FSM: Counter



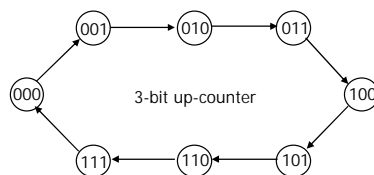- **Counters**
 - Proceed through a well-defined state sequence
- **Many types of counters: binary, Gray-code**
 - 3-bit up-counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, ...
 - 3-bit down-counter: 111, 110, 101, 100, 011, 010, 001, 000, 111, ...
- **Encoding of states: easy for counters – just use value**



	current state	next state
0	000	001 1
1	001	010 2
2	010	011 3
3	011	100 4
4	100	101 5
5	101	110 6
6	110	111 7
7	111	000 0





Ripple Counter (not synchronous)



Simple counter

- uses only registers (e.g., 74HC393 uses T-FF and negative edge-clocking)
- Toggle rate fastest for the LSB

  ...but ripple architecture leads to large skew between outputs



Possible implementation problems

- Many programmable fabrics require all clock inputs to be driven by special global clock signals



Structural VHDL Model for Ripple Counter



```

library ieee;
use ieee.std_logic_1164.all;

entity counter is
  port (clk : in std_logic;
        clear : in std_logic;
        count : out std_logic_vector(3 downto 0));
end counter;

architecture structural of counter is

  component d_ff
    port (clk : in std_logic;
          clear : in std_logic;
          d : in std_logic;
          q : out std_logic;
          nq : out std_logic);
  end component;

  signal ncount : std_logic_vector(3 downto 0);

begin

  ... (cont. on next viewgraph)

```

Include the model for a D Edge-Triggered Register

- The entity `d_ff` must be defined in the file `d_ff.vhd`



Structural VHDL Model (cont.)



```

bit_0 : d_ff
port map (clk => clk,
          clear => clear,
          d => ncount(0),
          q => count(0),
          nq => ncount(0));
bit_1 : d_ff
port map (clk => ncount(0),
          clear => clear,
          d => ncount(1),
          q => count(1),
          nq => ncount(1));
bit_2 : d_ff
port map (clk => ncount(1),
          clear => clear,
          d => ncount(2),
          q => count(2),
          nq => ncount(2));
bit_3 : d_ff
port map (clk => ncount(2),
          clear => clear,
          d => ncount(3),
          q => count(3),
          nq => ncount(3));
end structural;

```

Uses named association instead of positional association.
i.e., bit_0 : d_ff port map (clk, ncount(0), count(0), ncount(0));

Describes how the flip-flops are wired together

Implementation directly mimics the hardware in the previous slide

How do we model the D-FF?



Modeling Sequential Logic using Process



```

[label:] process [(sensitivity_list)]
[declarations]
begin
  {sequential_statement}
end process [label];

```

- A process is a wrapper for sequential statements
 - Sequential statements model combinational and synchronous logic
- When one of the signal in the *sensitivity list* changes, the sequential statements in the process are executed in sequence one time.
- Multiple processes are possible within an architecture. A process is concurrent with other concurrent statements.



Concurrent vs. Sequential Statements



```
A <= B;
B <= C;
C <= D;
```

```
process (B, C, D)
begin
  A <= B;
  B <= C;
  C <= D;
end process;
```

T	δ	A	B	C	D	comments
0	+0	1	2	3	0	
1	+0	1	2	3	4	3 executes
1	+1	1	2	4	4	2 executes
1	+2	1	4	4	4	1 executes
1	+3	4	4	4	4	No further execution

T	δ	A	B	C	D	comment
0	+0	1	2	3	0	
1	+0	1	2	3	4	1,2,3 execute; update A,B,C one delta later
1	+1	2	3	4	4	1,2,3 execute; update A,B,C one delta later
1	+2	3	4	4	4	1,2,3 execute; update A,B,C one delta later
1	+3	4	4	4	4	No further execution

During simulation, the scheduling and assigning of signal happens with a period known as simulation delta (delta cycle)



Modeling a D Flip-Flop in VHDL



```
library ieee;
use ieee.std_logic_1164.all;

entity d_ff is
  port ( clk : in std_logic;
        clear : in std_logic;
        d : in std_logic;
        q : out std_logic;
        nq : out std_logic);
end d_ff;

architecture behavioral of d_ff is

begin
  process (clear, clk)
  begin
    if clear = '1' then
      q <= '0';
      nq <= '1';
    elsif clk'event and clk = '1' then
      q <= d;
      nq <= not(d);
    end if;
  end process;
end behavioral;
```

- Sequential Logic is described using processes
- The entire body of a process executes in one delta of simulation time
- Individual processes are like individual concurrent statements and execute simultaneously



Anatomy of a Process



```
process (clear, clk) ←  
begin  
  if clear = '1' then  
    q <= '0';  
    nq <= '1';  
  elsif clk'event and clk = '1' then  
    q <= d;  
    nq <= not(d);  
  end if;  
end process;
```

Sensitivity list:

Contains a list of signals that trigger the process

- The process body is evaluated each time one of the signals in the sensitivity list changes state
- Most processes contain at least the global clock and reset signals in their sensitivity lists
- The sensitivity list is NOT used for synthesis



Anatomy of a Process



```
process (clear, clk) ←  
begin  
  if clear = '1' then  
    q <= '0';  
    nq <= '1';  
  elsif clk'event and clk = '1' then  
    q <= d;  
    nq <= not(d);  
  end if;  
end process;
```

Variable declarations
(if any)

- Processes may optionally define their own local variables
- Variables are updated when a sequential statement is executed.
- Signals are SCHEDULED to be updated when a statement is executed



Anatomy of a Process




```
process (clear, clk)
begin
  if clear = '1' then
    q <= '0';
    nq <= '1';
  elsif clk'event and clk = '1' then
    q <= d;
    nq <= not(d);
  end if;
end process;
```

**Sequential
statements**

- Body of process consists of sequential statements
- Statements are executed in order each time process is run



Ripple Counter Simulation (MAX+plusII)

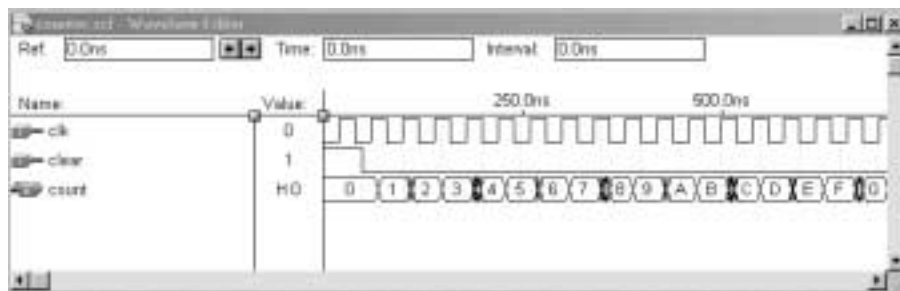

Notice the ripple effect and glitching



Using Wait Statements



- Wait statements delays the execution of the process until expression becomes true
- No *wait* statements allowed in the body if there is a sensitivity_list
- wait until (boolean_expression);
wait on (signal_name {,signal_name});
wait for (for time_expression);
- A simple D-FF

```
process
begin
  wait until (clk'event and clk='1');
  q <= d;
  nq <= not(d);
end process;
```



Sequential Statements



Some example sequential statements:

Assignment

```
<name> <= <value>; -- for signals
<name> := <value>; -- for variables
```

If statements

```
if <condition> then
  <statements>
elsif <condition> then
  <other statements>
else
  <statements>
end if;
```

} Optional but recommended

Case statements

```
case <signal/variable> is
  when <value1> => <statements>
  when <value2> => <statements>
  ...
  when others => <statements>
end case;
```

- Absence of *else* may result in implicit memory (if all possible conditions are not specified).
- Conditions do not have to be mutually exclusive.

- *when* clauses must be mutually exclusive.
- Always use a *when others* at the end



Inferring Latches vs. Registers



- Latches are level-sensitive and are much less common than registers
- Latches are often inferred by mistake, when what is desired is a register

```

process (c)
begin
  if c'event and c = '1' then
    q <= d;
  end if;
end process;

```

This infers a register.

Note that the *if* statement only executes when a transition occurs on *c*.

```

process (c)
begin
  if c = '1' then
    q <= d;
  end if;
end process;

```

This infers a latch.

The *if* statement executes whenever *c* is high.



Synchronous Counter Implementation



- D flip-flop for each state bit
- Combinational logic based on encoding

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

$$N1 := \overline{C1}$$



$$N2 := C1 \overline{C2} + \overline{C1} C2$$

$$:= C1 \text{ xor } C2$$

$$N3 := C1 C2 \overline{C3} + \overline{C1} C3 + \overline{C2} C3$$

$$:= C1 C2 C3 + (\overline{C1} + \overline{C2}) C3$$

$$:= (C1 C2) \text{ xor } C3$$

  


From [Katz93]



Implementing with T-FF



QC	QB	QA	NC	NB	NA	TC	TB	TA
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

 

Decide to implement with Toggle Flip-flops

What inputs must be presented to the T FFs to get them to change to the desired state bit?




This is called "Remapping the Next State Function"




With Toggle Inputs




K-maps for Toggle Inputs:

   

Resulting Logic Circuit:

 


Timing Diagram:

 

From [Katz93]



Catalog Counter: 74163

 

74163 Synchronous
4-Bit Upcounter

Synchronous Load and Clear Inputs

Positive Edge Triggered FFs

Parallel Load Data from D, C, B, A


P, T Enable Inputs: both must be asserted to enable counting

**RCO: asserted when counter enters its highest state 1111, used for cascading counters
"Ripple Carry Output"**

CLR and LOAD are synchronous
If CLR = 0 then Q:= 0
Else if LOAD then Q:= D
Else if P * T = 1 then Q:= Q + 1
Else Q:=Q




74163 (courtesy TI)

 




Counter Modes

 

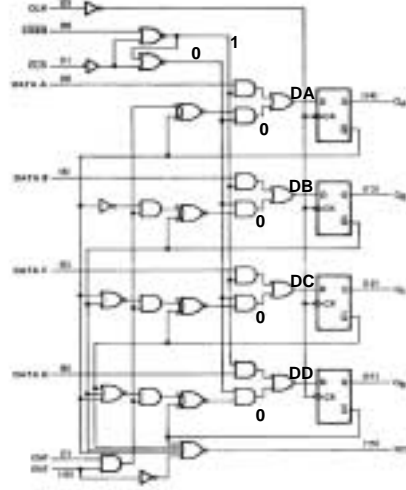
$\overline{\text{CLR}} = 0, \overline{\text{LOAD}} = 0$




$\overline{\text{CLR}} = 1, \overline{\text{LOAD}} = 0$



Counter Modes (cont.)

 

 
$\overline{\text{CLR}} = 1, \overline{\text{LOAD}} = 1, \text{PT} = 0$



$\overline{\text{CLR}} = 1, \overline{\text{LOAD}} = 1, \text{PT} = 1$



74163 Detailed Timing Diagram

 

L6: 6.111 Spring 2003

Introductory Digital Systems Laboratory

From [Katz93]

23



VHDL for 74163



```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity c74163 is
  port (LDN, CLRN, P, T, CLK: in std_logic;
        D : in std_logic_vector (3 downto 0);
        count : out std_logic_vector (3 downto 0);
        RCO : out std_logic);
end c74163;

architecture behavior of c74163 is
  signal Q: std_logic_vector (3 downto 0);
begin
  count <= Q;
  RCO <= Q(3) and Q(2) and Q(1) and Q(0) and T;

  process
  begin
    wait until (CLK'event and CLK = '1');
    if CLRN = '0' then Q <= "0000";
    elsif LDN = '0' then Q <= D;
    elsif (P and T) = '1' then Q <= Q + 1;
    end if;
  end process;
end architecture behavior;
  
```

- Our entire counter example can be defined in one process
 - Behavioral, rather than structural specification
 - Synthesis tools will map behavior to logic
 - This is the more typical style of coding


L6: 6.111 Spring 2003

Introductory Digital Systems Laboratory

24



Simulation

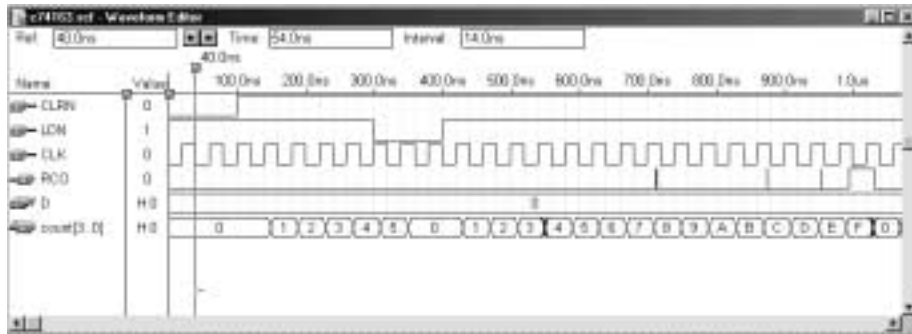



There should be no glitches on the output (ideally)



Output Transitions



  
- Anytime multiple bits change, the counter output needs time to settle
- Even though all flip-flops share the same clock, individual bits will change at different times
 - Clock skew, propagation time variations
- Can cause glitches in combinational logic driven by the counter



All of these transitions paths are possible!




Cascading 74163s (the wrong way)

 

- '163 is enabled only if P and T are high
- RCO goes high when '163 is about to roll over to 0000
- Connecting RCO to P makes second '163 increment once whenever first '163 rolls over
- P on first '163 is connected to master enable



Cascading 74163s (the right way)

 


- '163 is enabled only if P and T are high
- RCO goes high when '163 is about to roll over to 0000
- Connecting RCO to P makes second '163 increment once whenever first '163 rolls over
- P on first '163 is connected to master enable



Counter Tricks




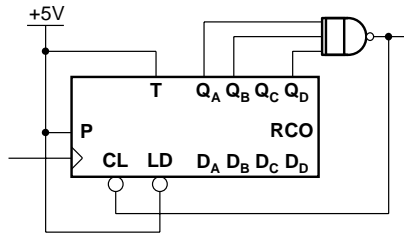Configured to automatically reset at 1011



Counts 0000, 0001, ..., 1010,
1011, 0000, ...

Configured to automatically load 0100

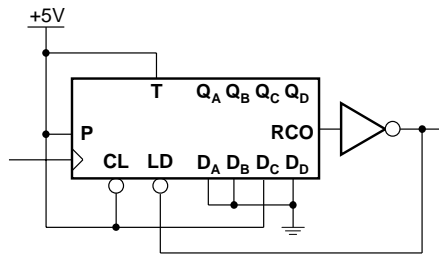

Counts 0100, 0101, ..., 1110,
1111, 0100, ...



Up/Down Counter with enable



```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity updowncounter is
port (clk : in std_logic;
      reset : in std_logic;
      up : in std_logic;
      enable : in std_logic;
      count : out std_logic_vector (3 downto 0));
end updowncounter;



architecture structural of updowncounter is
signal Q : std_logic_vector (3 downto 0);
begin

count <= Q;

process (clk, reset)
begin
if reset = '1' then
Q <= (others => '0');
elsif clk'event and clk = '1' then
if enable = '1' and up = '1' then
Q <= Q + 1;
elsif enable = '1' and up = '0' then
Q <= Q - 1;
end if;
end if;
end process;

end structural;

```

 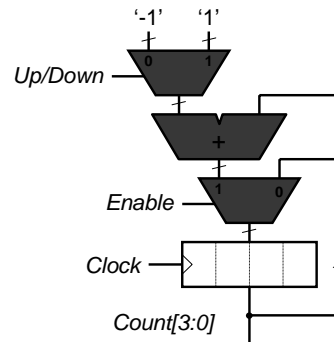




The Up/Down Counter as an FSM



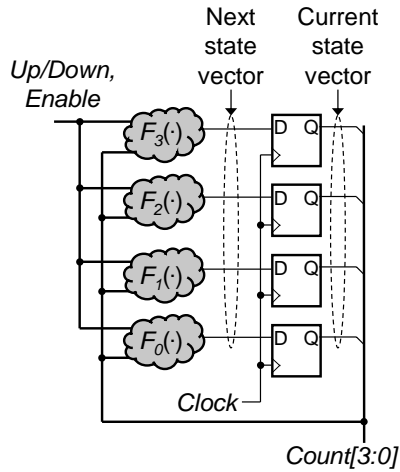Next state functions $F_0(), \dots, F_3()$ are derived from a state transition table



Partial state transition table

Inputs		Current State				Next State			
U/D	E/n	C_0	C_1	C_2	C_3	C_{+0}	C_{+1}	C_{+2}	C_{+3}
...
0	1	0	0	0	0	1	1	1	1
0	1	1	0	0	0	0	0	0	0
0	1	0	1	0	0	1	0	0	0
0	1	1	1	0	0	0	1	0	0
1	1	0	0	1	0	1	1	0	0
1	1	1	0	1	0	0	0	1	0
1	1	0	1	1	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0
...

Karnaugh-maps, Boolean algebra, etc... used to simplify and implement state transition functions.