



L7: Memory Basics and Timing



Acknowledgement: Nathan Ickes



Memory Classification & Metrics




Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E ² PROM	Mask-Programmed
SRAM DRAM	FIFO LIFO	FLASH	

Key Design Metrics:

1. Memory Density (number of bits/ μm^2) and Size
2. Access Time (time to read or write) and Throughput
3. Power Dissipation




Memory Array Architecture

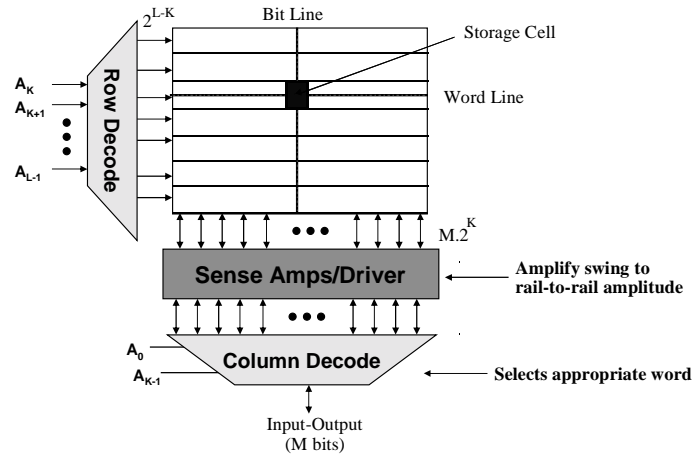


Latch and Register Based Memory



Positive Latch Negative Latch

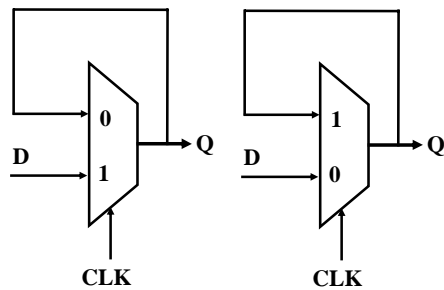

Register Memory

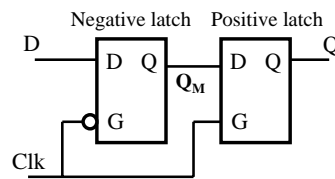


- Works fine for small memory blocks (e.g., small register files)
- Inefficient in area for large memories – density is the key metric in large memory circuits

How do we minimize cell size?




Static RAM (SRAM) Cell (The 6-T Cell)

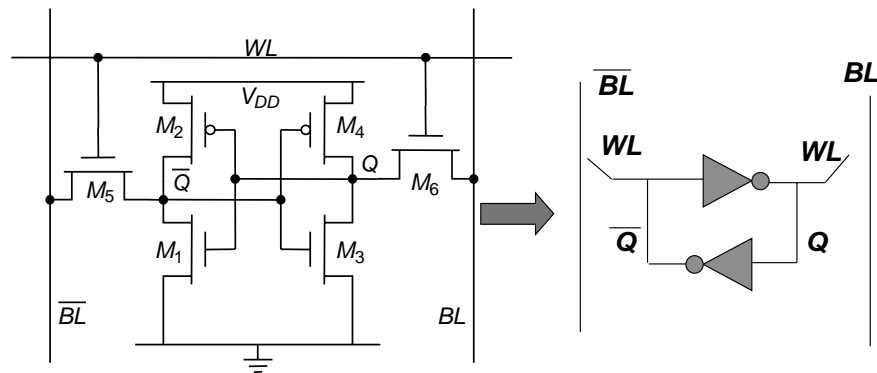

- State held by cross-coupled inverters (M1-M4)
- Retains state as long as power supply turned on
- Feedback must be overdriven to write into the memory



Dynamic RAM (DRAM) Cell

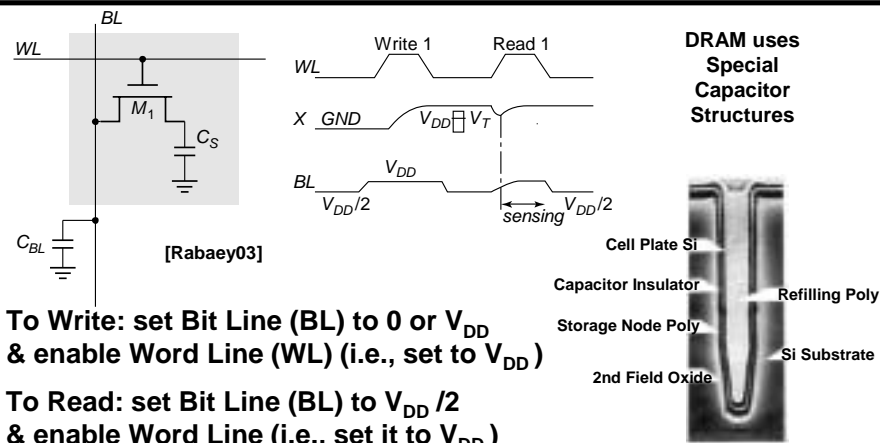


DRAM uses Special Capacitor Structures

To Write: set Bit Line (BL) to 0 or V_{DD} & enable Word Line (WL) (i.e., set to V_{DD})


To Read: set Bit Line (BL) to $V_{DD}/2$ & enable Word Line (i.e., set it to V_{DD})

- DRAM relies on charge stored in a capacitor to hold state
- Found in all high density memories (one bit/transistor)
- Must be “refreshed” or state will be lost – high overhead

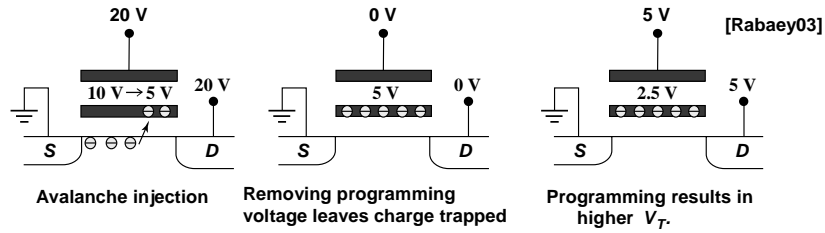EPROM Cell – The Floating Gate Transistor





EPROM Cell
Courtesy Intel

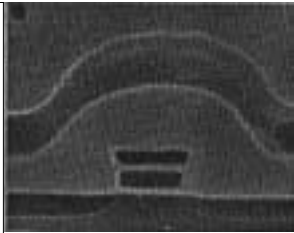

This is a non-volatile memory (retains state when supply turned off)

Density/Size Memory Trends

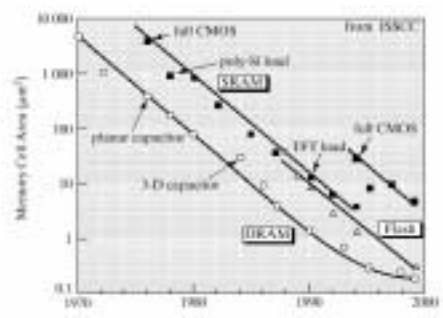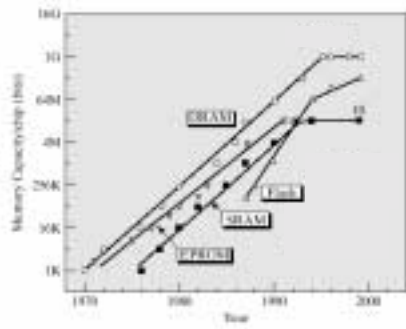

From [Itoh01]



Key Messages on Memory Devices




- **SRAM vs. DRAM**
 - SRAM holds state as long as power supply is turned on. DRAM must be “refreshed” – results in more complicated control
 - DRAM has much higher density, but requires special capacitor technology.
 - FPGA usually implemented in a standard digital process technology and uses SRAM technology
- **Non-Volatile Memory**
 - Fast Read, but very slow write (EPROM must be removed from the system for programming!)
 - Holds state even if the power supply is turned off
- **Memory Internals**
 - Has quite a bit of analog circuits internally -- pay particular attention to noise and PCB board integration
- **Device details**
 - Don't worry about them, wait until 6.012, 6.371 or 6.374



MCM6264C 8k x 8 Static RAM




- **Same (bidirectional) data bus used for reading and writing**
- **Chip Enables ($\overline{E1}$ and $E2$)**
 - $\overline{E1}$ must be low and $E2$ must be high to enable the chip
- **Write Enable (\overline{W})**
 - When low (and chip is enabled), the values on the data bus are written to the location selected by the address bus
- **Output Enable (\overline{G})**
 - When low (and chip is enabled), the data bus is driven with the value of the selected memory location

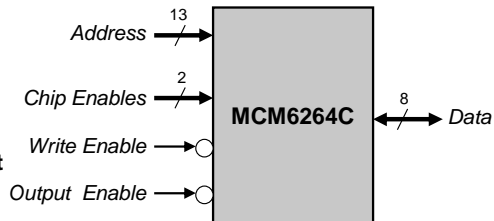


HE0	0	00	VCC
A0	1	01	W
A0	2	01	W
A0	3	01	W
A0	255	01	W



Inside the '6264C

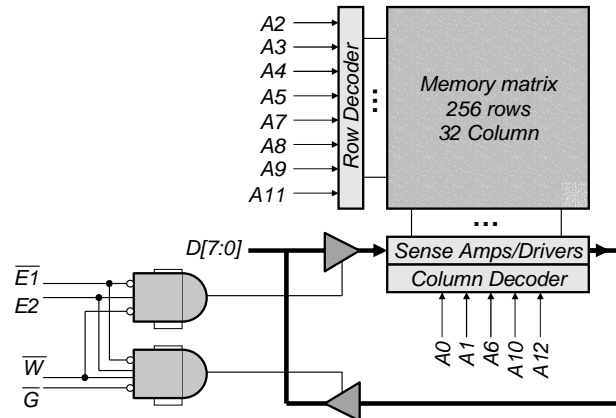


Reading From SRAM

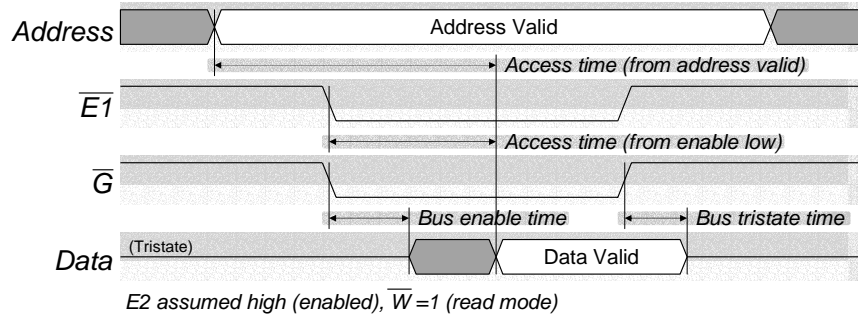

- Read cycle begins when all enable signals ($\overline{E1}$, $E2$, \overline{G}) are active
- Data is valid after read access time
 - Access time is indicated by full part number: MCM6264CP-12 \rightarrow 12ns
- Data bus is tristated shortly after \overline{G} or $\overline{E1}$ goes high




Address Controlled Reads

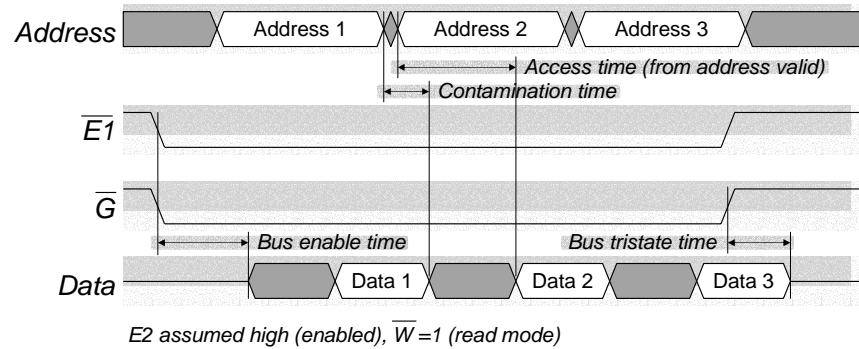

- Can perform multiple reads without disabling chip
- Data bus follows address bus, after some delay



Writing to SRAM

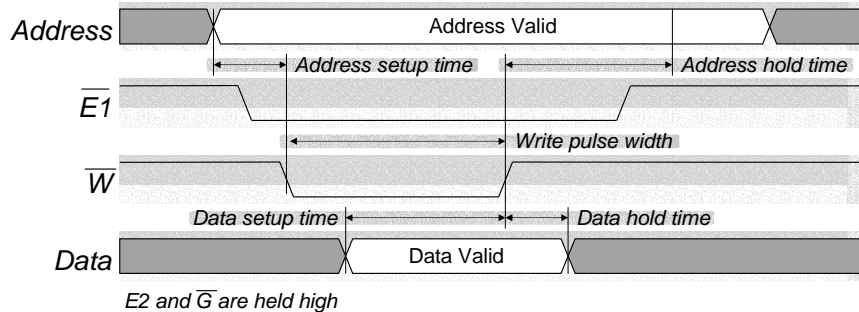

- Data latched when \bar{W} or $\bar{E1}$ goes high (or E2 goes low)
 - Data must be stable at this time
 - Address must be stable before \bar{W} goes low
- Write waveforms are more important than read waveforms
 - Glitches can cause writes to random addresses!




Flash and (E)EPROM




- Reading from flash or (E)EPROM is the same as reading from SRAM
- Vpp: input for programming voltage (12V)
 - EPROM: Vpp is supplied by programming machine
 - Modern flash/EEPROM devices generate 12V using an on-chip charge pump
- EPROM lacks a write enable
 - Not in-system programmable (must use a special programming machine)
- For flash and EEPROM, write sequence is controlled by an internal FSM
 - Writes to device are used to send signals to the FSM
 - Although the same signals are used, one can't write to flash/EEPROM in the same manner as SRAM


Flash/EEPROM block diagram

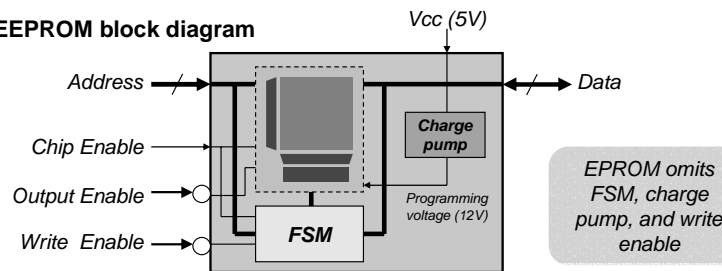

Sample Memory Interface Logic

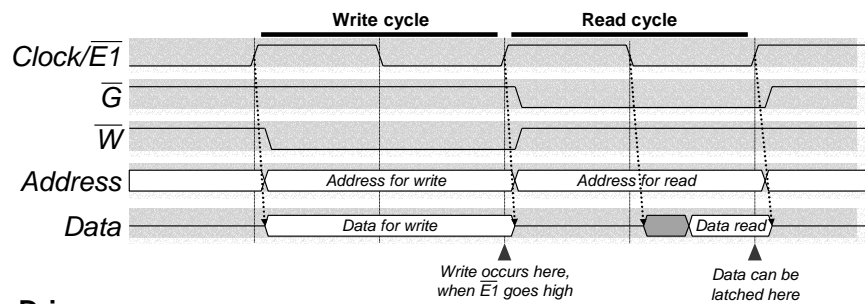

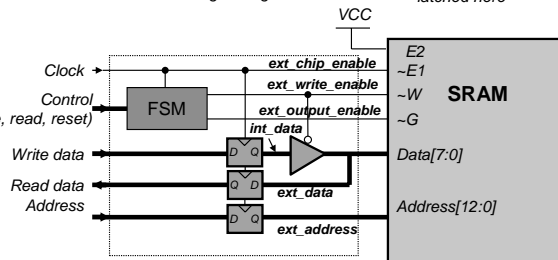- Drive memory enable with clock
 - Ensures data and memory busses are stable for writes
 - Minimum clock period is twice memory access time





Toy Memory Interface in VHDL (I)



```
library ieee;
use ieee.std_logic_1164.all;

entity mem_int is
  port (clock : in std_logic;
        reset : in std_logic;
        write : in std_logic;
        read : in std_logic;
        address : in std_logic_vector(12 downto 0);
        write_data : in std_logic_vector(7 downto 0);
        read_data : out std_logic_vector(7 downto 0);
        ext_chip_enable : out std_logic;
        ext_write_enable : out std_logic;
        ext_output_enable : out std_logic;
        ext_address : out std_logic_vector(12 downto 0);
        ext_data : inout std_logic_vector(7 downto 0));
end mem_int;

architecture behavioral of mem_int is

  signal int_data : std_logic_vector(7 downto 0);

  (cont. on next viewgraph)
```



Toy Memory Interface in VHDL (II)



```
begin
  ext_chip_enable <= clock;
  ext_data <= int_data when ext_write_enable = '0' else (others => 'Z');

  process (clock, reset)
  begin
    if reset = '0' then
      ext_write_enable <= '1';
      ext_output_enable <= '1';
    elseif clock'event and clock = '1' then
      ext_address <= address;
      read_data <= ext_data;
      int_data <= write_data;
      if write = '1' then
        ext_write_enable <= '0';
      elseif read = '1' then
        ext_output_enable <= '0';
      else
        ext_write_enable <= '1';
        ext_output_enable <= '1';
      end if;
    end if;
  end process;



end behavioral;
```



Creating Larger Memories



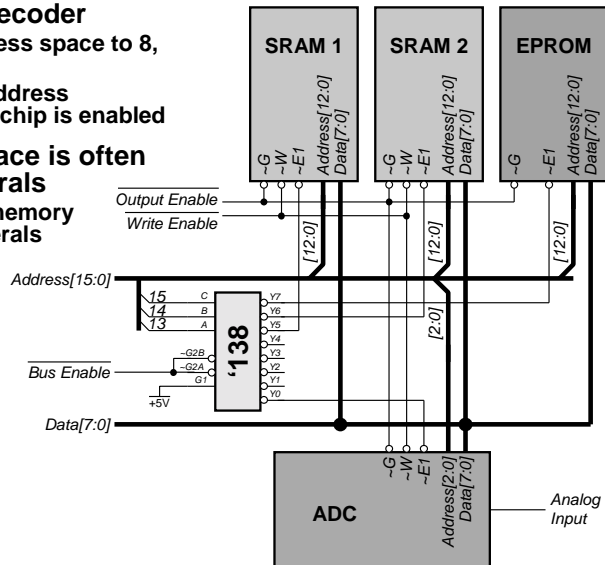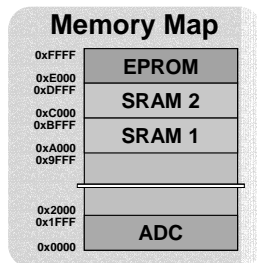- '138 is a 3-to-8 decoder
 - Maps 16 bit address space to 8, 13 bit segments
 - Upper 3 bits of address determine which chip is enabled
- SRAM-like interface is often used for peripherals
 - Referred to as "memory mapped" peripherals



L7: 6.111 Spring 2003

Introductory Digital Systems Laboratory

19



Testing Memories



- **Common device problems**
 - Bad locations: rare for individual locations to be bad
 - Slow (out-of-spec) timings: causes intermittent failures
 - Catastrophic device failure: e.g., ESD
 - Missing wire-bonds/devices (!): possible with automated assembly
 - Transient Failures: Alpha particles, power supply glitch
- **Common circuit problems**
 - Stuck-at-Faults: a pin shorted to VDD or GND
 - Open Circuit Fault: connections unintentionally left out
 - Open or shorted address wires: causes data to be written to incorrect locations
 - Open or shorted control wires: generally renders memory completely inoperable

L7: 6.111 Spring 2003

Introductory Digital Systems Laboratory

20



Testing Memory




- Since device problems generally affect the entire chip, almost any test will detect them
- Writing (and reading back) many different data patterns can detect data bus problems
- Writing unique data to every location and then reading it back can detect address bus problems



Testing Memory



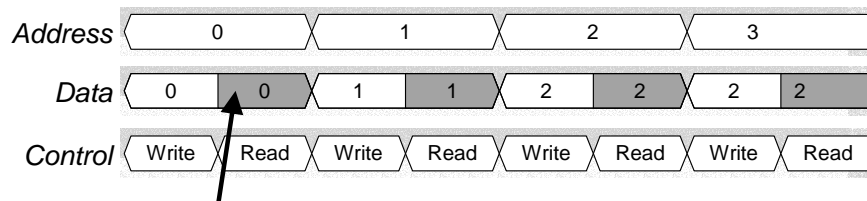- An idea that almost works
 1. Write 0 to location 0
 2. Read location 0, compare value read with 0
 3. Write 1 to location 1
 4. Read location 1, compare value read with 1
 5. ...
- What is the problem?
 - Suppose the memory was missing (or output enable was disconnected)



Data bus is undriven but wire capacitance briefly maintains the bus state: memory appears to be ok!




Testing Memory



Write to all locations, then read back all locations

- Separates read/write to the same location with reads/writes of different data to different locations
- (both data and address busses are changed between read and write to same location)

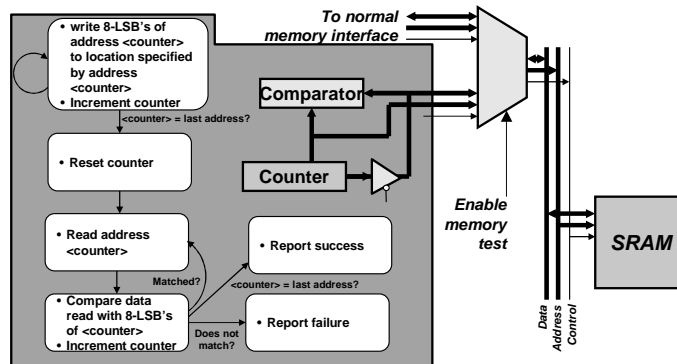- Write 0 to address 0
- Write 1 to address 1
- ...
- Write ($n \bmod 256$) to address n
- Read address 0, compare with 0
- Read address 1, compare with 1
- ...
- Read address n , compare with ($n \bmod 256$)



Multi-Port Memories




Applications

- Register files, FIFO, buffer, etc.

Cypress CY7C132 2kx8 dual port SRAM

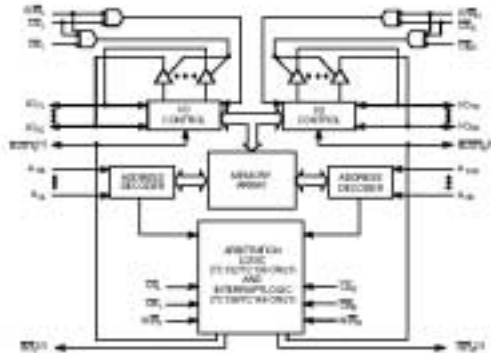- Two independent, asynchronous read/write ports
- Can access two different memory locations simultaneously
- Busy signal indicates if both ports attempt to access same location at the same time






Building a FIFO




- Head pointer: points to next available location for writing
- Tail pointer: points to next available location for reading
- If head and tail pointers are the same, FIFO is empty
- If $head+1 = tail$, FIFO is full
- Pointers wrap around when they reach the end of the memory


Empty

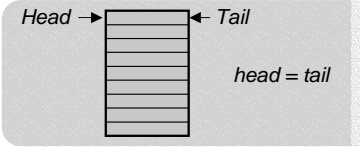

After 4 writes and 2 reads

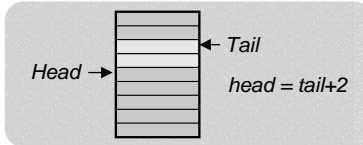

Full

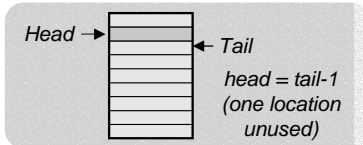

Building a FIFO

