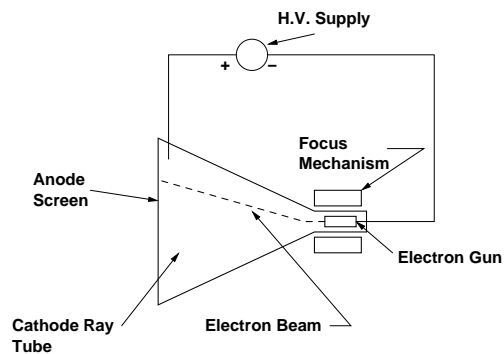


**Video**

Video 6.111 Introductory Digital Systems Laboratory <sub>1</sub>

## Video Displays

- Video displays are implemented by mirrors, LCDs, and CRTs.
- In a CRT (the displays in our laboratory)
  - electron beams are focused on a small spot on the screen.
  - The energy delivered to a phosphor causes a dot (pixel) to glow.
  - The beam can be moved rapidly in two dimensions.
  - The beam current determines the brightness of the spot.






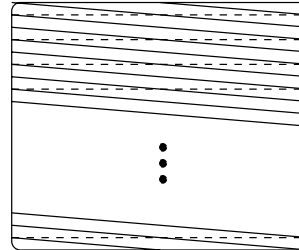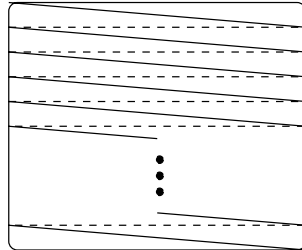
# Raster Scan



- Television and most computer displays use raster scan.



Non-Interlaced: Frame rate may be 60, 72, etc. frames/sec.

———— Scan line  
 - - - - - Retrace line

Interlaced: Frames alternate.  
 This is like television: 60 half frames/sec.

Electron beam "scans" tube. Beam location is shown here. Beam current determines brightness of display.

Video 6.111


Introductory Digital Systems Laboratory 3



# Composite Frames



- The 'frame' is a single picture (snapshot).
  - It is made up of many lines.
  - Each frame has a synchronizing pulse (vertical sync).
  - Each line has a synchronizing pulse (horizontal sync).
  - Brightness is represented by a positive voltage.
  - Horizontal and Vertical intervals both have blanking so that retraces are not seen (invisible).

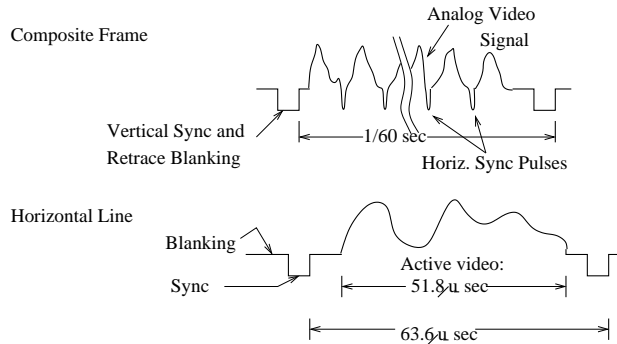

Video 6.111


Introductory Digital Systems Laboratory 4



## Synchronization



- The picture consists of white dots on a black screen.
  - White is the highest voltage.
  - Black is a low voltage.
  - Sync is below the black voltage.
- Sync pulses are surrounded by the blanking interval so one doesn't see the retrace.

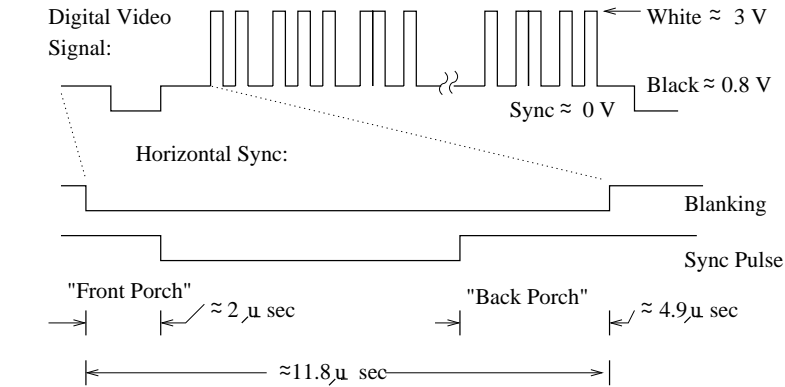

Video 6.111


Introductory Digital Systems Laboratory 5



## Composite Synchronization



- Horizontal sync coordinates lines.
- Vertical sync coordinates frames.
- They are similar except for the time scales and they are superimposed on each other. The numbers are for TV-like displays.
  - What purpose is there for serrated sync?

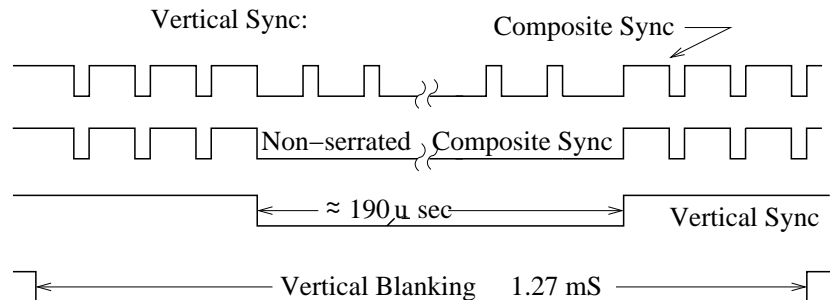

Video 6.111


Introductory Digital Systems Laboratory 6



## (Conceptual) Recovery of Signals



- Composite video has picture data and both syncs.
  - Picture data (video) is above the sync level.
  - Simple comparators extract video and composite sync.
- Composite sync is fed directly to the horizontal oscillator.
- A low-pass filter is used to separate the vertical sync.
  - The edges of the low-passed vertical sync are squared up by a Schmidt trigger.

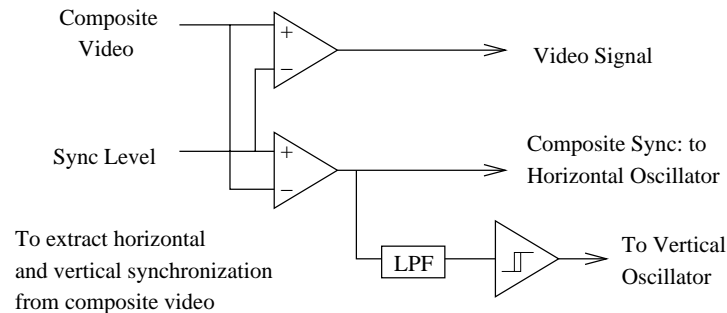


Video 6.111



## Generation of Signals



- Assume one bit per pixel and provide for reverse video.
- This is a simple 'D/A' to generate monochrome signals.
  - The 'S38 is an open collector part so the voltages are determined by the resistor network. The output resistance is ~ 75 ohms.

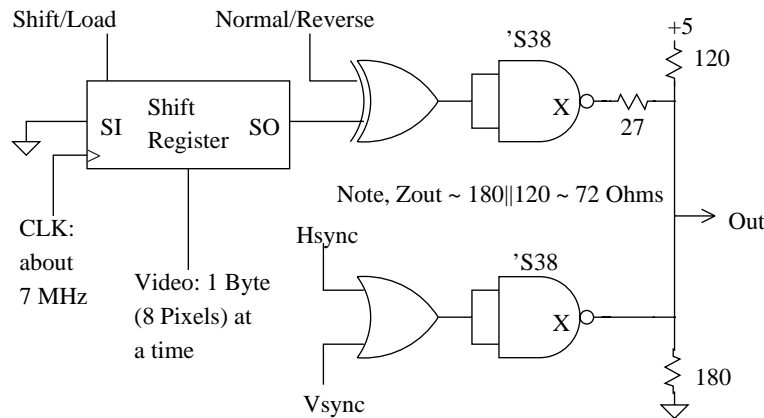


Video 6.111



## Control



- Here is one possible display format.
  - 256 pixels X 192 rows
  - 7.16 MHz clock => 140 nanoseconds per pixel
  - Display time for the active line is 35.8 microseconds.
  - $256 \times 192 = 49,152 = 48\text{K pixels} = 6 \text{ K bytes}$

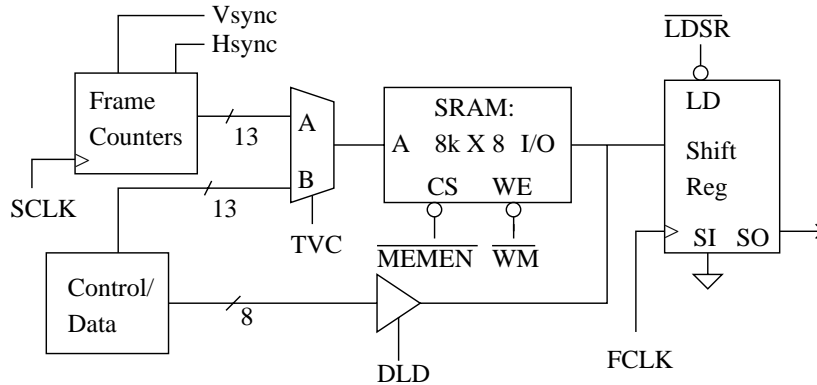

Video 6.111


Introductory Digital Systems Laboratory 9



## Timing of Control Signals



- Data is loaded into a shift register and shifted out to generate the video signal.
  - FCLK is at the pixel rate.
  - TVC divides access to the SRAM giving half the time to get data to load into the shift register .

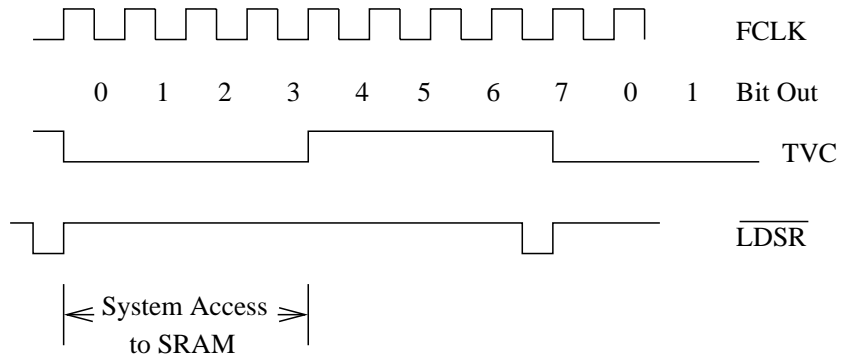

Video 6.111


Introductory Digital Systems Laboratory 10



## Generation of Control Signals



- Here is one way to generate control signals
  - by storing information in ROMs to generate sync signals, TVC, and /EOL.
  - Note that EOL cause a line count and /EOL clears the dot counter.
  - And that (EOF AND EOL) causes a clear of the line counter.

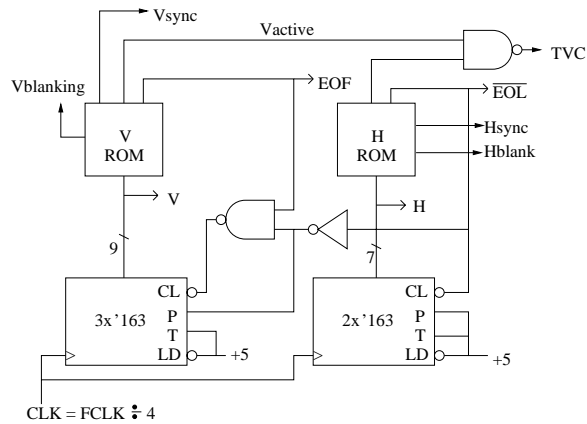

Video 6.111

Introductory Digital Systems Laboratory 11



## ROM Contents for Control



### ■ Vertical Rom

Number of words	Addresses	Contents
192	0 - 191	Vactive
26	192 - 217	Vblanking
6	218 - 223	Vsync
37	224 - 260	Vblanking
1	261	EOF

### ■ Horizontal ROM

Number of words	Addresses	Contents
32	0 - 31	Hactive
9	32 - 40	Hblanking
7	41 - 47	Hsync
8	48 - 55	Hblanking
1	56	EOL

- Whoops! Make sure the EOL bit is negative true.

Video 6.111


Introductory Digital Systems Laboratory 12



## Color Displays



- Color displays are similar to three monochrome displays operated together, i.e., the colors add.
- Three binary signals yield an eight-color display.
  - Some monitors have an analog video input for each color.
- Sync is sometimes on a separate wire.
  - Sometimes it is superimposed on the green signal.

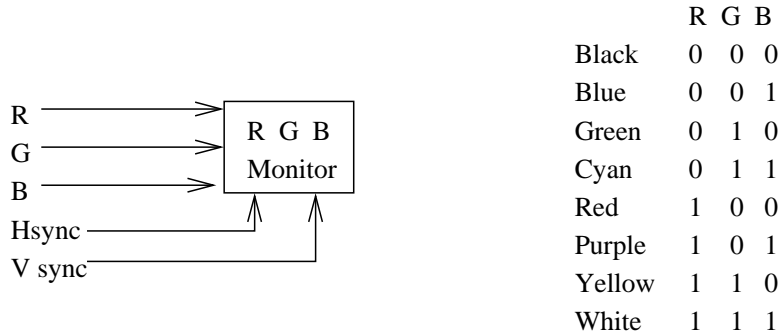

Video 6.111

Introductory Digital Systems Laboratory 13




## Character Display (8 x 16 pixels)



- Characters are fixed bit patterns.
  - They always have the same shape but can appear at different places on the screen.
  - Use of characters can save video memory and make the manipulation of video memory contents simpler.

For a screen 256 x 192 one gets 384 characters. The screen address is used to specify the position and part of the address of the character ROM

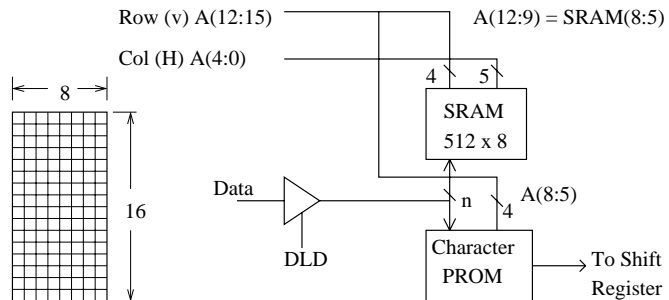

Video 6.111

Introductory Digital Systems Laboratory 14




## Character Displays (8 x 12 pixels)



- Row formatting is not as simple as before.
  - But remapping is easily done in a prom or VHDL.

For a screen 256 x 192 one gets 512 characters. The screen address modified by combinational logic is used to specify the position and part of the address of the character ROM

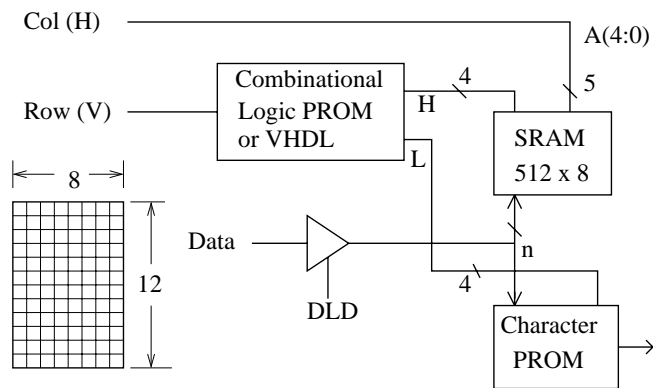

Video 6.111


Introductory Digital Systems Laboratory 15



## Pairs of Characters



- Sometimes, pairs of characters can create the same motion effect as bit-mapped graphics.
  - The speed of the motion depends on the update rate.
- These 24 characters (12 x 2) can display an arrow at any vertical position.

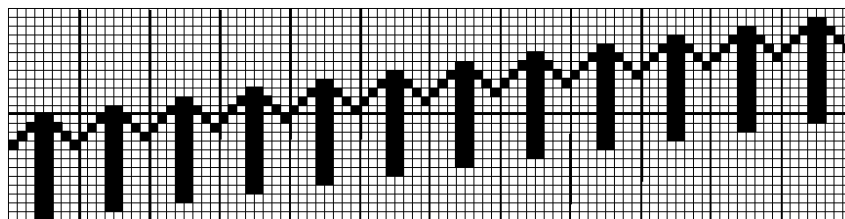

Video 6.111


Introductory Digital Systems Laboratory 16



## Video Controllers



- MC6847 is obsolete but easy to use.
  - It provides a 13-bit address and an analog video signal.
  - It reads 8-bit data which can be either a character code or video data.
  - Several display modes include 256 x 192 two-color and several other color graphics modes with lower resolution.

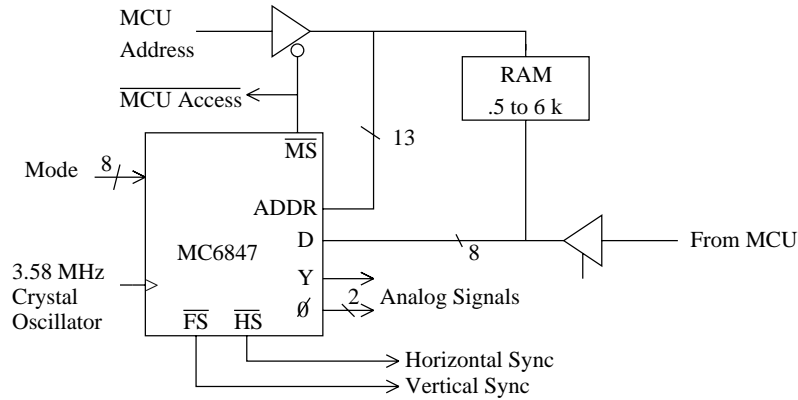

Video 6.111


Introductory Digital Systems Laboratory 17



## Bit-Mapped Video



- MC6847 can be used with bit-mapped video.
  - More about Y, phi A, and phi B later.

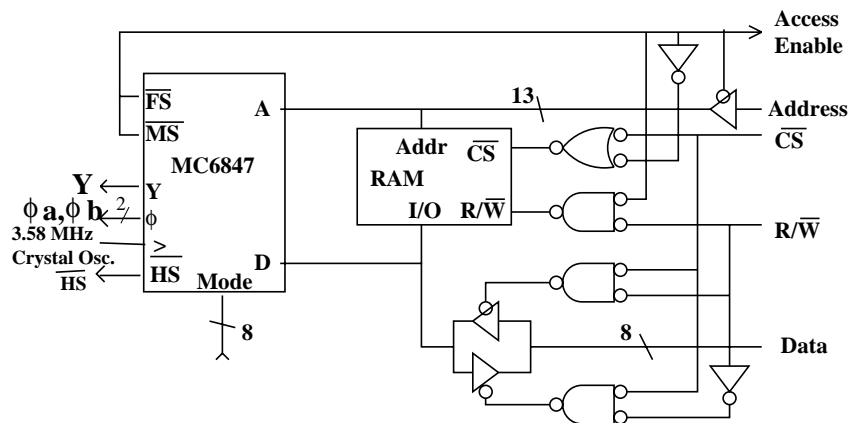

Video 6.111

Introductory Digital Systems Laboratory 18






## Centering the Display



- The MC6847 generates blanking, not vertical sync.
- You have to generate vertical sync.
  - You can do this digitally with counters.
  - Alternatively, one can use two one-shots.
    - The first one-shot triggers on the falling edge of /FS and determines the delay of Vsync.
    - The second one-shot determines the width of Vsync.
    - Adjust the pots so that the picture is centered on the monitor.

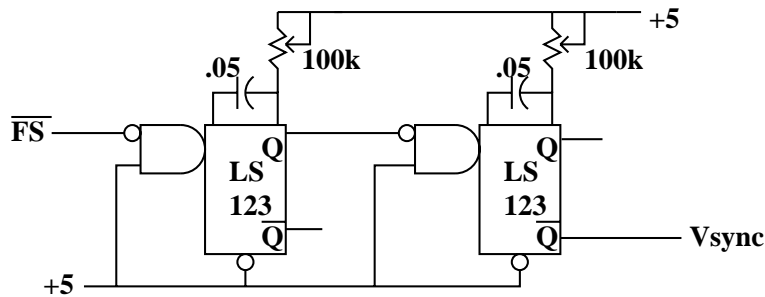

Video 6.111


Introductory Digital Systems Laboratory 21



## Drive a Monitor



- Use a 75 ohm coax cable to connect to the monitor.
  - Remember to terminate the monitor with 75 ohms.
    - There is usually a switch on the back of the monitor.
- Here is a simple way to drive a monochrome monitor.
  - Don't make the gain of the '357 too small or you will get some ringing.
  - The Y output has composite sync and luminance.

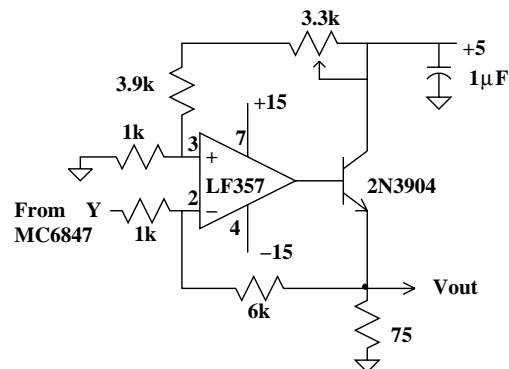

Video 6.111


Introductory Digital Systems Laboratory 22



## Color Output



- The first step is to convert the analog signals, phi A and phi B, to digital signals.
- The circuit on the right works for one of the color modes. It is not guaranteed to work for the mode you want to use!
  - In particular, the luminance signal may never be a one for your mode.
  - Display a test pattern and look at the analog signals with a scope.
- The resistor chain determines the voltages input to the comparators (as in a flash converter).
- The AM26LS32 is a “fast” comparator (it is actually a line receiver).

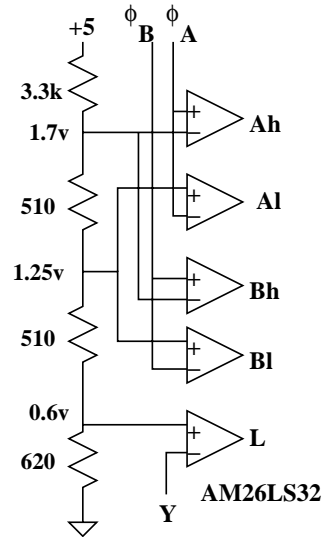

Video 6.111

Introductory Digital Systems Laboratory 23




## Coding to Get RGB



- This combinational logic can (should) be implemented in VHDL.
- The logic depends on the mode selected.
  - Look at the Ah, Al, Bh, Bl, and L outputs to determine the logic needed.
  - The 74S38 driving the 620 ohm resistor is one way to get orange.

An available cable pinout is:

Pin 1	Intensity
Pin 2	Red
Pin 3	Green
Pin 4	Blue
Pin 5	GND
Pin 6	GND
Pin 7	HSYNC
Pin 8	VSYNC

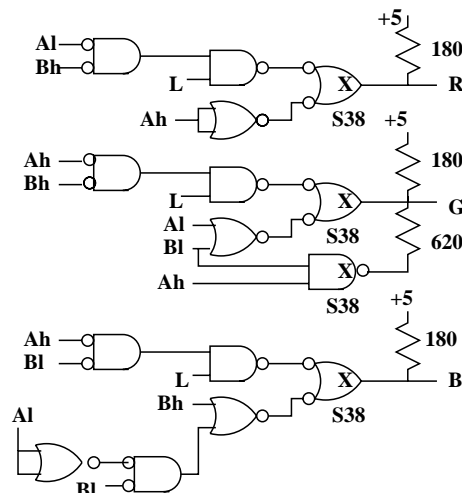

These Drive RGB Inputs

Video 6.111

Introductory Digital Systems Laboratory 24