




Motors and Position Determination



Controlling Position



- Feedback is used to control position.
 - Measure the position, subtract a function of it from the desired position and then use this resulting signal to drive the system towards the desired position. This is negative feedback.
 - The natural frequencies of the feedback system are the “zeros” of $1 + G(s)H(s)$.
 - The total system is unstable if these “zeros” are in the right half plane (RHP). With 180 degrees phase shift, “negative” feedback becomes “positive” feedback.
 - So we want these “zeros” to be in the left half plane (LHP).
 - Putting an integrator into $H(s)$ drives steady state error to zero.
 - But high order systems are more likely to have RHP zeros.
 - Time delay and high gain lead to RHP zeros.

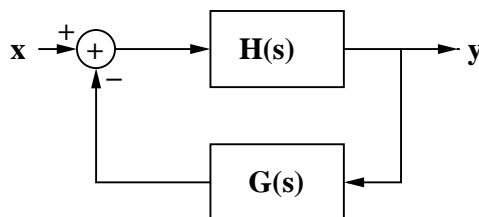


$$\frac{Y(s)}{X(s)} = \frac{H(s)}{1 + G(s)H(s)}$$



Servos



- We can control parts of the servo, but the system dynamics is often a part we can't control.
 - The system dynamics results from masses, springs, losses, etc.
- Likely, we will implement servos as digital systems.
 - Digital systems are more flexible to design.
 - They are more repeatable; they are not subject to gain drift.
 - We can use as many bits as we like so we can keep the computation noise small.
 - Digital systems can have significant delays.
 - These delays are sometimes fixed, but are sometimes stochastic.

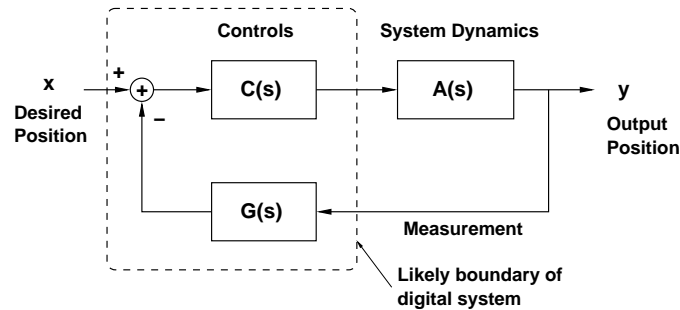

Motors 6.111

Introductory Digital Systems Laboratory 3




Analog Position Measurements



Voltage is proportional to position.

A linear or rotary potentiometer can be used.

Accuracy is limited to that of the potentiometer and the noise of the power supply voltage.

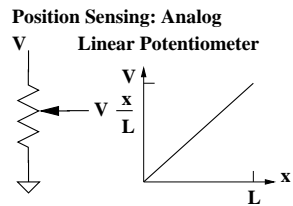

Motors 6.111


Two sinusoidal potentiometers are used.

$$V_1 = V_0 \cos(\theta)$$

$$V_2 = V_0 \sin(\theta)$$

This can also be done magnetically.

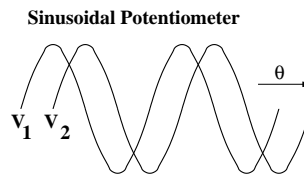This is called a resolver and requires a complex analog signal detection. The computation can be done with either analog or digital circuitry.




Introductory Digital Systems Laboratory 4



Digital Position Measurement



- Sense light transmission to determine position.
 - Typically through a transparent sector
 - Gives a reading over a range of positions.
 - Depends on extent of transparent sector.
 - One may need a lot of sensors to determine multiple positions.

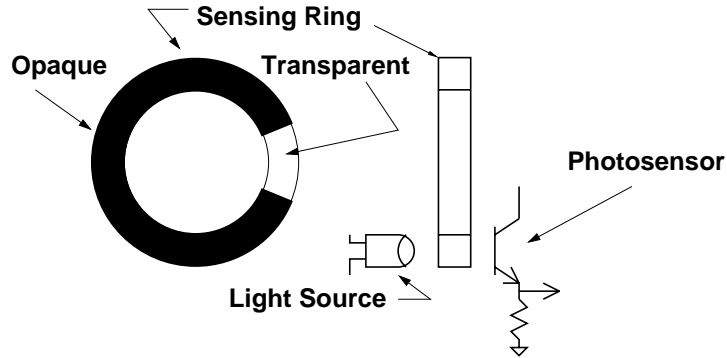

Motors 6.111


Introductory Digital Systems Laboratory 5



Digital Absolute Position



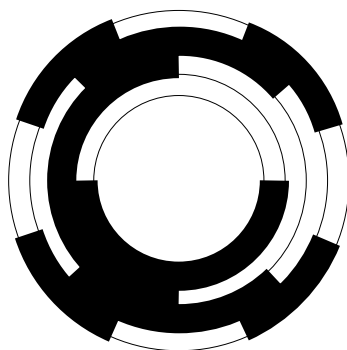- Typically, this is used for relatively low resolutions.



Here is a 4-bit (22.5 degree)
resolution wheel.
One source per sensor
bit

Can make these wider.
Resolution is

$$\frac{360^{\circ}}{2^N}$$

Use a Gray Code to
eliminate chatter.

0	0	0	0
0	0	0	1
0	0	1	1
0	0	1	0
0	1	1	0
0	1	1	1
0	1	0	1
0	1	0	0
1	1	0	0
1	1	0	1
1	1	1	1
1	1	1	0
1	0	1	0
1	0	1	1
1	0	0	1
1	0	0	0

Motors 6.111


Introductory Digital Systems Laboratory 6



Two-Phase Encoder



- Two Source – Sensor Sets
 - Their position is offset by half the sector width.
 - This example has 30 degree sectors
 - and 15 degree resolution.

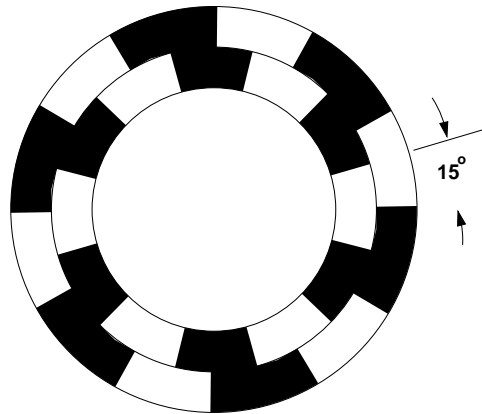

Motors 6.111


Introductory Digital Systems Laboratory 7



Use of Two-Phase Encoder



- This circuit generates:
 - An Up/Down signal depending on whether the motion is clockwise (CW) or counterclockwise (CCW).
 - A clk signal which rising edge is to operate the counter.

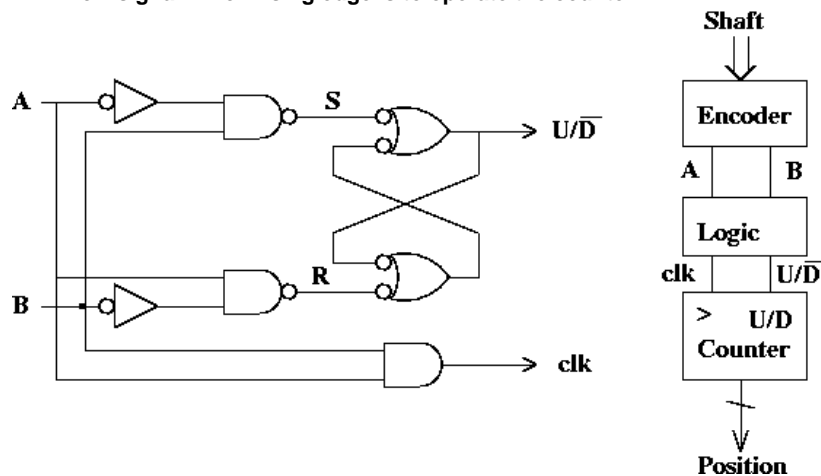

Motors 6.111


Introductory Digital Systems Laboratory 8



Waveforms



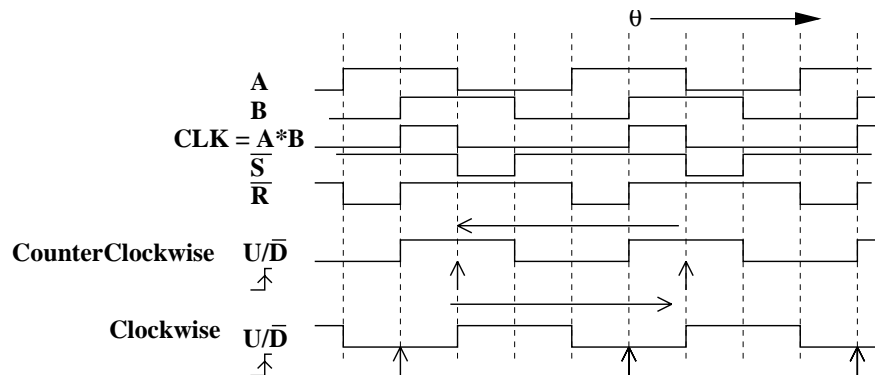
- A and B are signals derived from sensors.
- Rotating one way, the rising edge of clk is when U/D is high.
- Rotating the other way, the rising edge of clk is when U/D is low.



Another Way of Making an Encoder



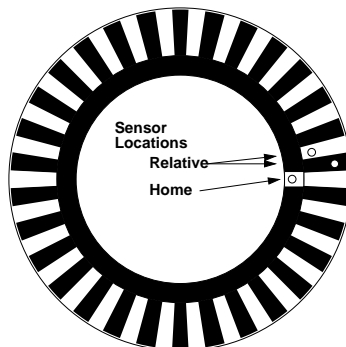- Use two sensors like the two-phase encoder but use only one ring and displace the sensors by $\frac{1}{2}$ band.
- Add another ring and a sensor to sense the “home” position.






Motors



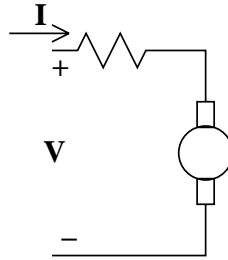- Simple servomechanisms are made with DC motors.
 - DC motor model is very simple:
 - It consists of a resistor in series with a voltage source.
 - The voltage source is proportional to the rotational speed.
 - The mechanical system (controlled system) determines the speed as influenced by the torque.



$$V = G \Omega + R I$$


$$\text{Torque } T = G I$$



Permanent Magnet DC Motors



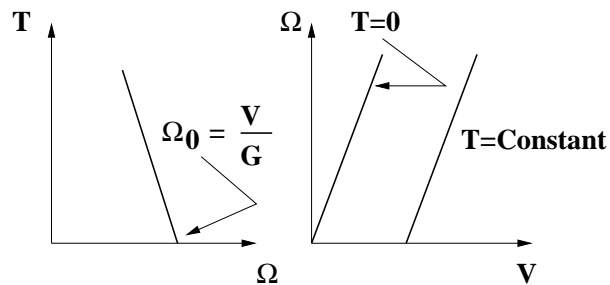- They are very commonly used.
 - The 'Back Voltage' is proportional to speed.
 - The torque is proportional to the current.
- Servo Strategy:
 - Command torque by setting current.
 - Measure the speed.
- Running open loop:
 - There is a 'zero torque' speed.
 - Torque is proportional to the difference from that speed.







Stepper Motors



- Digital Motors
 - Two 'stacks' (phases)
 - Usually biased by permanent magnets
 - Move a discrete distance per 'step'.
 - This is an axial view cut through both of two sections.

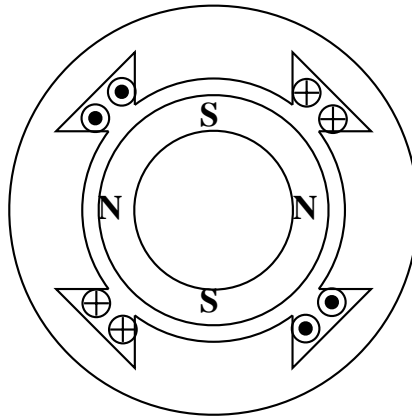

Motors 6.111

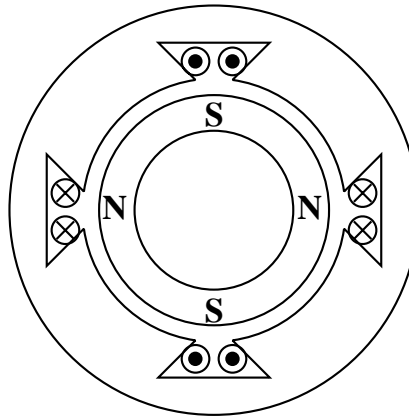


Introductory Digital Systems Laboratory 13




Stepper Motor Windings



- Two distinct 'phases'
 - May be driven as distinct windings.
 - Or may be driven as 'bifilar' windings.
 - Bifilar is easier but less efficient.

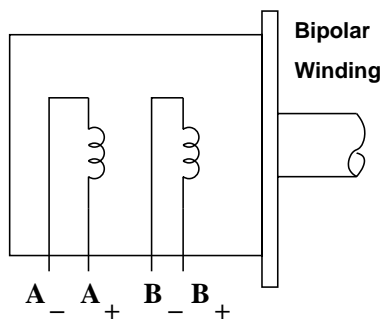

Motors 6.111

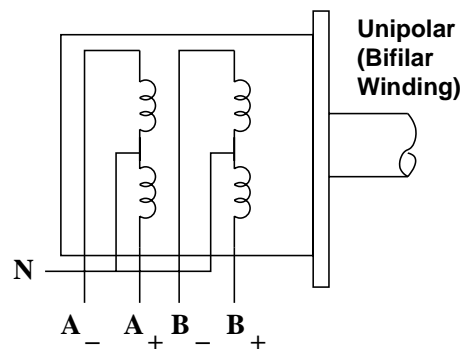



Introductory Digital Systems Laboratory 14



Bipolar Winding



- Driven by 'H-bridges' of transistors
 - Can put current through windings in either direction.
 - But note that the upper transistor drive is tricky.
 - Uses all of the winding.

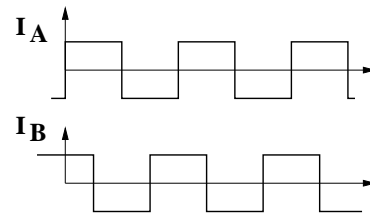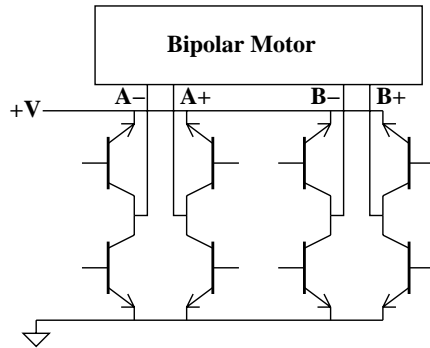

Motors 6.111



Introductory Digital Systems Laboratory 15



Bifilar Winding



- Driven by four transistors to ground.
 - Note that the center of the windings is held high.
 - Transistors are between winding and ground.
 - NPN bipolar transistors work well.
 - Transistor drives are easily handled.

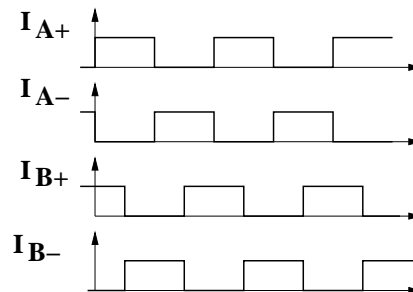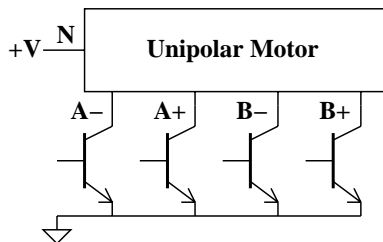

Motors 6.111

Introductory Digital Systems Laboratory 16



Motors Run in Either Direction



- Current drive strategy:

Bipolar Winding

Step	I_A	I_B
1	+	+
2	+	-
3	-	-
4	-	+

Clockwise ↓ (next to Step 1-2)
 Counter-Clockwise ↑ (next to Step 3-4)

Bifilar Winding

Step	I_{A+}	I_{A-}	I_{B+}	I_{B-}
1	1	0	1	0
2	1	0	0	1
3	0	1	0	1
4	0	1	1	0


Clockwise ↓ (next to Step 1-2)
 Counter-Clockwise ↑ (next to Step 3-4)



Dynamics are Important



- Stepper can hold a certain torque.
- Stepper can carry more torque at low speed.
- At high speed, torque must be de-rated.
- Motors draw **CURRENT!** Make sure your power supply is adequate by measuring the power supply voltage with a 'scope.
 - Use an external supply, not the kit supply.
 - You don't want motor drive noise in your digital circuit (or analog circuit).
- You need to make sure that devices can handle the current and torque.

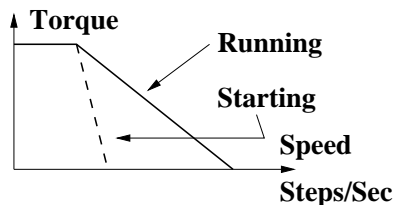

Must sometimes 'ramp up' speed.
 Holding torque is limited by heating and by saturation.